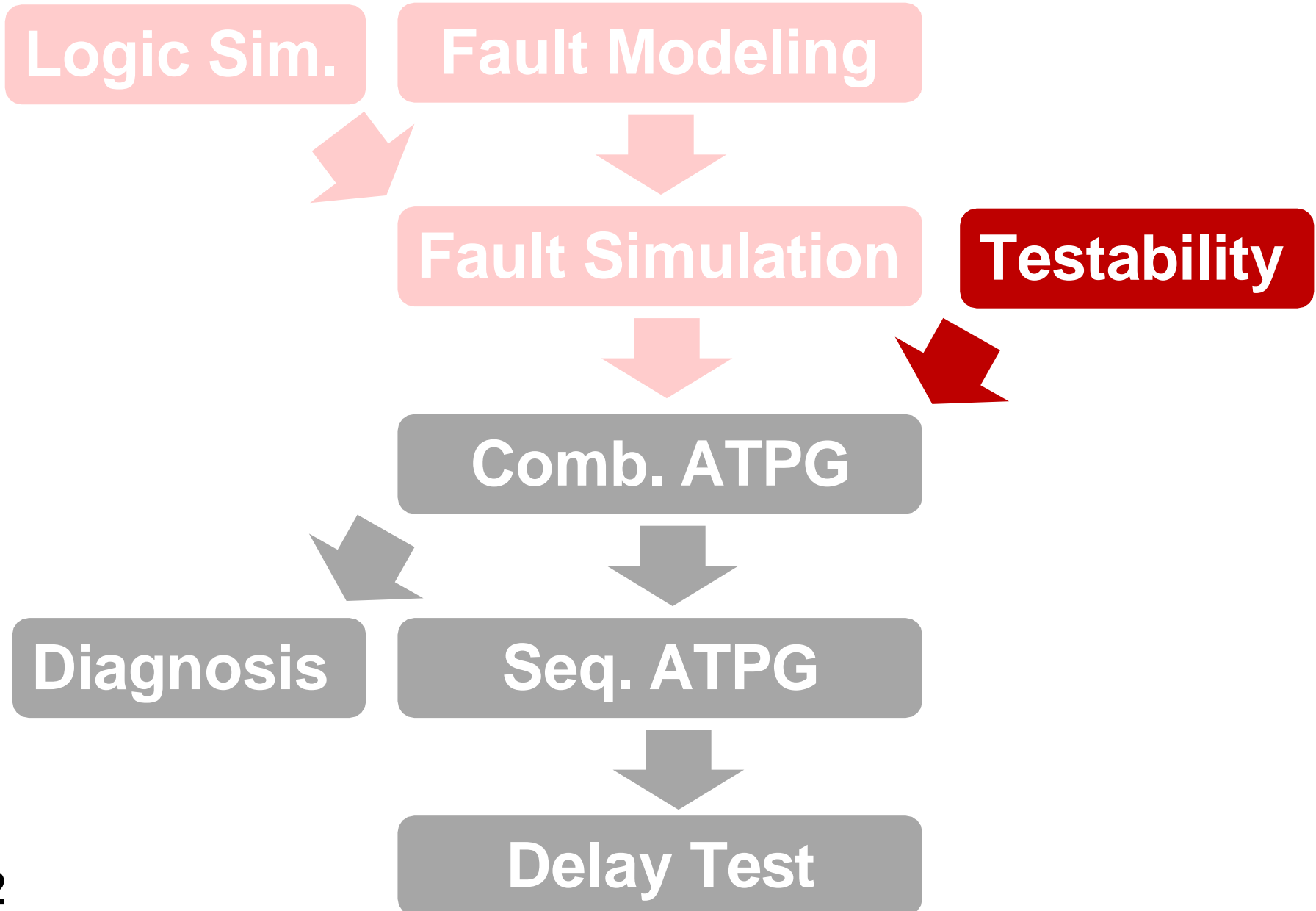


Testability Measures


Dr. Bharat Garg
Assistant Professor,
DECE, TIET, Patiala

Course Roadmap (EDA Topics)



Motivating Problem

 - You report fault coverage of test set to your manager. Your manager is not very happy about FC number. He asked you: which faults are so difficult to detect?



Why Am I Learning This?

- Testability measure helps to
 - ◆ Make smart decision in ATPG
 - ◆ More testable designs

“Measurement is the first step that leads to control and eventually to improvement. ”

(H. James Harrington)

Testability Measures

- What is testability measure?
 - ◆ Metric to measure degree of difficulty to test a circuit
- Two important components:
 - ◆ **Controllability**
 - * degree of difficulty to control a logic signal to 0 or 1
 - ◆ **Observability**
 - * degree of difficulty to observe the logic value of a signal

Testability Measures Controllability and Observability

Testability Analysis

- What is *Testability Analysis*?
 - ♦ Calculate testability measures for a given circuit
- Why testability analysis?
 - ♦ 1. **Help ATPG** make smart decision
 - ♦ 2. **Insert DFT** circuits to improve controllability and observability
- When testability analysis?
 - ♦ In *preprocess stage* of ATPG or DFT insertion
- Requirements of testability analysis
 - ♦ Should run very fast
 - ♦ Sometimes , accuracy is not very important

Categories of Testability Analysis

- 1. ***Topology-based*** analysis
 - ♦ Only analyzes structure of circuit. No test vectors are given.
 - ♦ Example: SCOAP
- 2. ***Probability-based*** analysis
 - ♦ Uses *signal probability* to estimate the testability
 - ♦ Example: COP
- 3. ***High-level*** analysis
 - ♦ Performs testability analysis before synthesis
 - ♦ Example: RTL testability analysis
- 4. ***Simulation-base*** analysis (not in lecture)
 - ♦ Apply input patterns,
 - ♦ Perform simulation and estimate testability

SCOAP [Goldstein 1979]

- ***Sandia Controllability Observability Analysis Program****
- SCOAP computes 6 numbers for each node N

*Sandia is name of research lab.

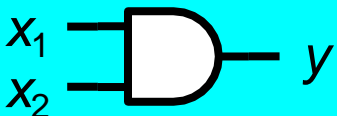
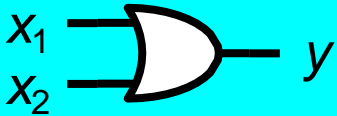

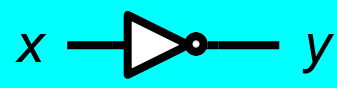
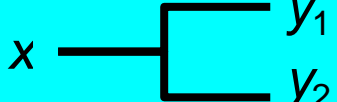
	0-controllability	1-controllability	Observability
Combinational	$CC^0(N)$	$CC^1(N)$	$CO(N)$
Sequential	$SC^0(N)$	$SC^1(N)$	$SO(N)$

Combinational Controllability

- $CC^0(N)$, $CC^1(N)$
 - ♦ minimum number of combinational PI assignments and logic levels required to control a 0 or a 1 on node N
 - ♦ *Smaller* number, *easier* to control
- How to calculate CC?
 - ♦ $CC(PI) = 1$.
 - ♦ From PI to PO. Add 1 to account for logic level
- Gate propagation rules:
 - ♦ If only one input controls gate output:
 - * $CC(\text{gate_output}) = \min \{ CC(\text{gate_input}) \} + 1$
 - ♦ If all inputs needed to set gate output:
 - * $CC(\text{gate_output}) = \sum CC(\text{gate_input}) + 1$
 - ♦ $CC(\text{branches}) = CC(\text{stem})$


Smaller CC is Better

CC⁰(N) & CC¹(N)

	CC ⁰ (y)	CC ¹ (y)
Primary inputs	1	1
	$\min[CC^0(x_1), CC^0(x_2)] + 1$	$CC^1(x_1) + CC^1(x_2) + 1$
	$CC^0(x_1) + CC^0(x_2) + 1$	$\min[CC^1(x_1), CC^1(x_2)] + 1$
	$\min[CC^0(x_1) + CC^0(x_2), CC^1(x_1) + CC^1(x_2)] + 1$	$\min[CC^0(x_1) + CC^1(x_2), CC^1(x_1) + CC^0(x_2)] + 1$
	$CC^1(x) + 1$	$CC^0(x) + 1$
	$CC^0(y_1) = CC^0(y_2) = CC^0(x)$	$CC^1(y_1) = CC^1(y_2) = CC^1(x)$


An Example – Controllability

- Forward: From PI to PO

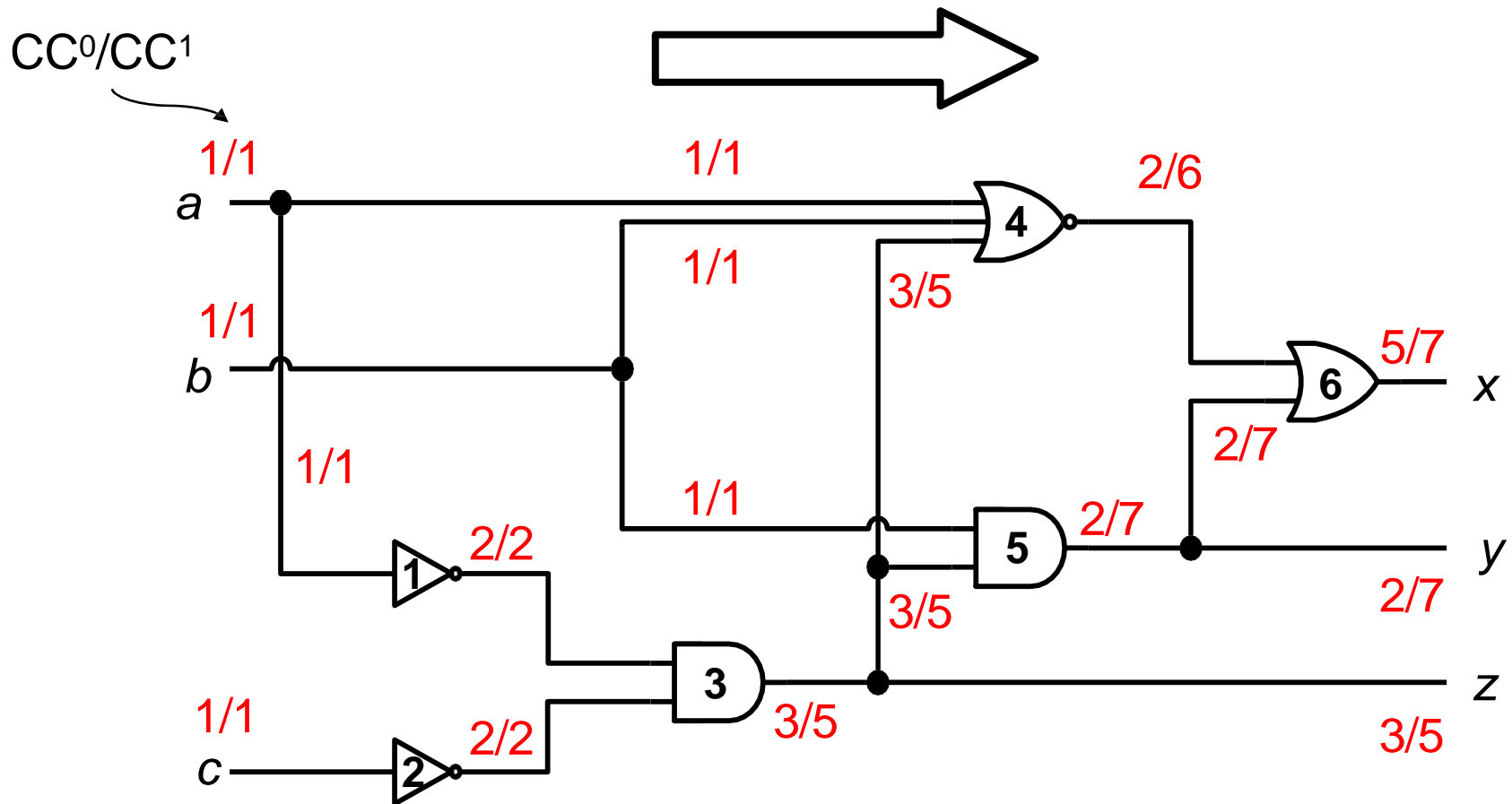

Quiz

 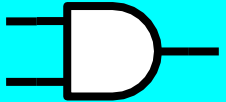
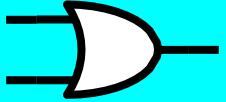

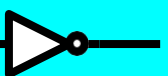
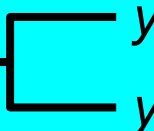
Q: how to control y to 0? How to control y to 1?



Combinational Observability


- $CO(N)$
 - ♦ minimum number of combinational PI assignments and logic levels required to propagate logical value on node N to PO
 - ♦ *Smaller* number, *easier* to observe
- How to calculate $CO(N)$?
 - ♦ $CO(PO)=0$
 - ♦ From POs to PIs, add 1 to account for logic level
- $CO(\text{gate_input}) = \Sigma$
 - ♦ (1) $CO(\text{gate_output})$
 - ♦ (2) $CC(\text{setting all other inputs to non-controlling value})$
 - ♦ (3) + 1 for logic level
- How about fanout stem? Assume they are *independent*
 - ♦ $CO(\text{stem}) = \min \{ CO(\text{branches}) \}$

CO(N)

	CO(x_1)
Primary outputs	0
x_1 x_2  y	$CO(y) + CC^1(x_2) + 1$
x_1 x_2  y	$CO(y) + CC^0(x_2) + 1$
x_1 x_2  y	$CO(y) + \min[CC^0(x_2), CC^1(x_2)] + 1$
x_1  y	$CO(y) + 1$
x_1  y_1 y_2	$\min[CO(y_1), CO(y_2)]$

An Example – Observability

- Backward: From PO to PI

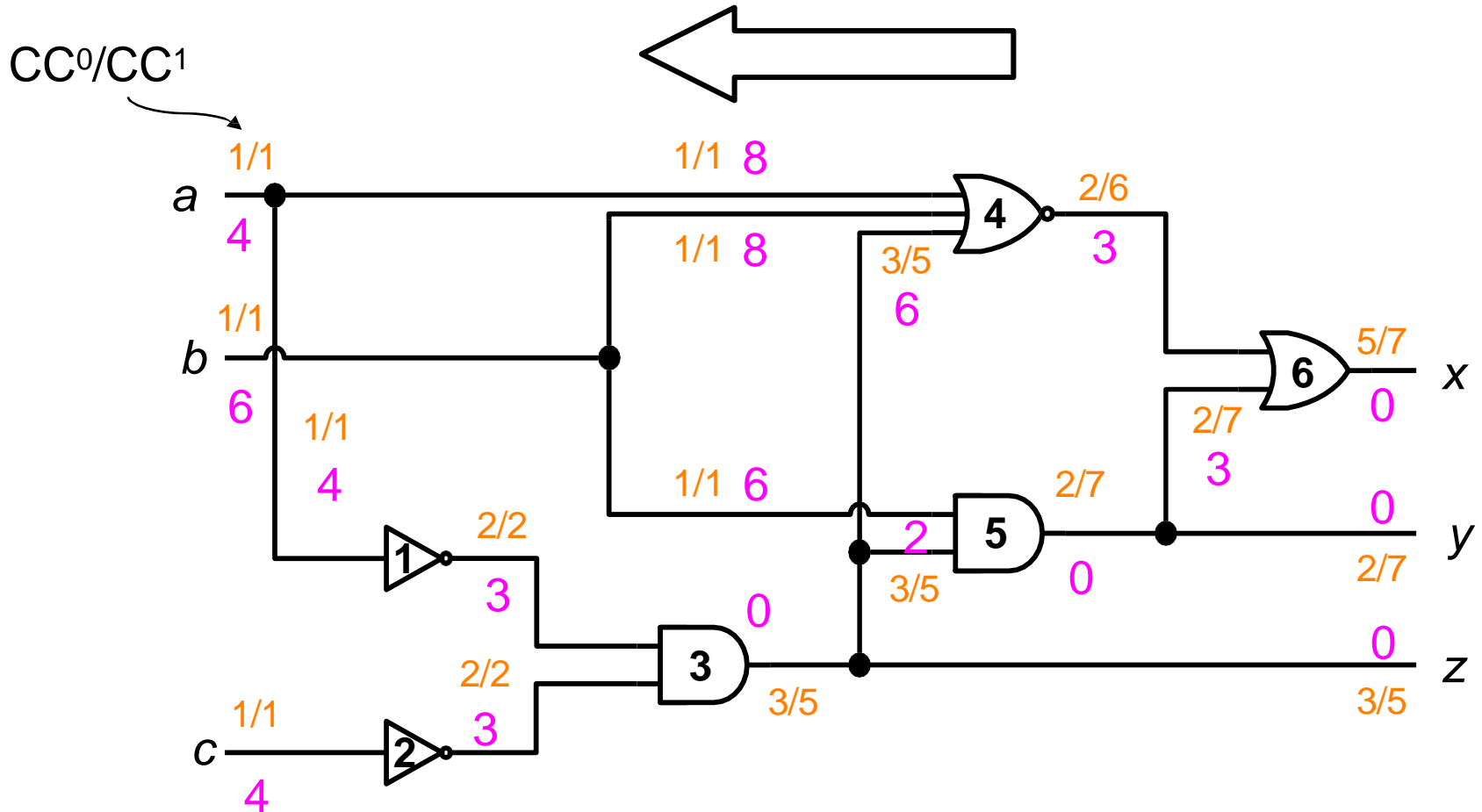


Quiz

Q: Please analyze combinational SCOAP.


A:

	A	B	C	E	F	L	H	J	K
CC ⁰									
CC ¹									
CO									

 

FFT

- Q: Testability should be done very quickly. What is time complexity to calculate CC and CO?

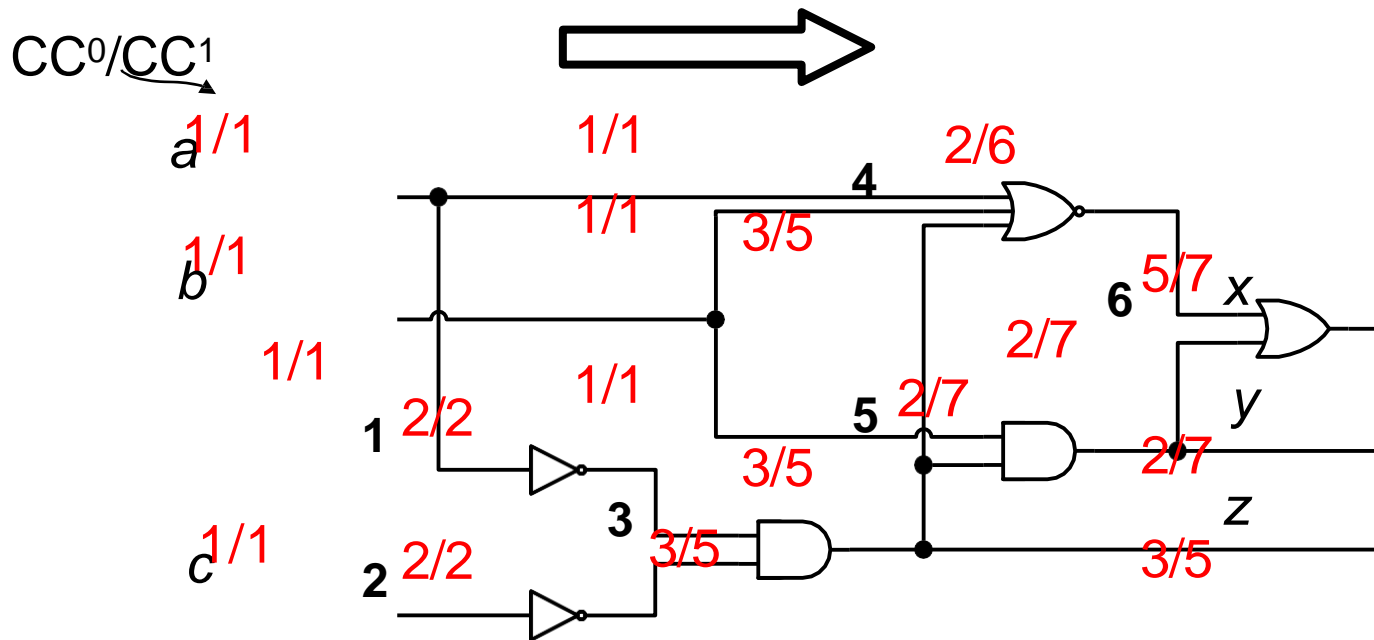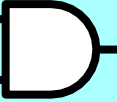
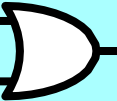

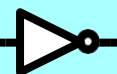
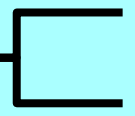


Sequential SCOAP Measures






- **Sequential controllability:** $SC^0(N)$, $SC^1(N)$
 - ♦ Minimum number of **FF assignments** (number of clock cycles) required to control 0 or 1 on node N
 - ♦ **smaller** number means **easier** to control
- **Sequential observability:** $SO(N)$
 - ♦ Minimum number of **FF assignments** required to propagate logical value on node N to a primary output
- **NOTE:** assume **no scan**
 - ♦ Can only control PI, observe PO
 - ♦ Can **NOT** control FF, can **NOT** observe FF

Sequential SCOAP Measures
of Clock Cycles Needed

SC⁰(N) and SC¹(N)


	SC ⁰ (y)	SC ¹ (y)
Primary inputs	0 (not 1)	0
x_1 x_2  y	$\min[SC^0(x_1), SC^0(x_2)]$ +1	$SC^1(x_1) + SC^1(x_2)$
x_1 x_2  y	$SC^0(x_1) + SC^0(x_2)$	$\min[SC^1(x_1), SC^1(x_2)]$
x_1 x_2  y	$\min[SC^0(x_1) + SC^0(x_2), SC^1(x_1) + SC^1(x_2)]$	$\min[SC^0(x_1) + SC^1(x_2), SC^1(x_1) + SC^0(x_2)]$
x  y	$SC^1(x)$	$SC^0(x)$
x_1  y_1 y_2	$SC^0(y_1) = SC^0(y_2) = SC^0(x_1)$	$SC^1(y_1) = SC^1(y_2) = SC^1(x_1)$

SO(N)

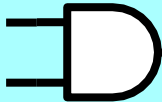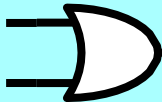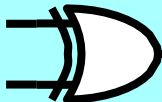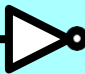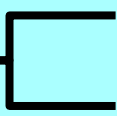	SO(x_1)
Primary outputs	0
x_1 x_2  y	SO(y) + SC ¹ (x_2) +1
x_1 x_2  y	SO(y) + SC ⁰ (x_2)
x_1 x_2  y	SO(y) + min[SC ⁰ (x_2), SC ¹ (x_2)]
x_1  y	SO(y)
x_1  y_1 y_2	min[SO(y_1), SO(y_2)]

Flip-Flop (Controllability)

 
- Positive edge triggered, asynchronous reset



$$\begin{aligned} CC^1(Q) &= CC^1(D) + CC^1(CLK) + CC^0(CLK) + CC^0(R) \\ SC^1(Q) &= SC^1(D) + SC^1(CLK) + SC^0(CLK) + SC^0(R) + 1 \end{aligned}$$

$$\begin{aligned} CC^0(Q) &= \min[CC^1(R), \\ &\quad CC^0(D) + CC^1(CLK) + CC^0(CLK) + CC^0(R)] \\ SC^0(Q) &= \min[SC^1(R), \\ &\quad SC^0(D) + SC^1(CLK) + SC^0(CLK) + SC^0(R)] + 1 \end{aligned}$$

Flip-Flop (Observability)

 


$$\begin{aligned} CO(D) &= CO(Q) + CC^1(CLK) + CC^0(CLK) + CC^0(R) \\ SO(D) &= SO(Q) + SC^1(CLK) + SC^0(CLK) + SC^0(R) + 1 \end{aligned}$$


Seq. SCOAP Computation Alg.

- Computation of SC, SO is similar to CC, CO
 - ◆ but require *iterations* for controllability to converge



Controllability:

1. For all PI's, set $CC^0 = CC^1 = 1$ and $SC^0 = SC^1 = 0$
2. For all other nodes, set $CC^0 = CC^1 = \infty$ and $SC^0 = SC^1 = \infty$
3. Propagate controllability from PI's to PO's 
Iterate until numbers stabilize.

Observability:


1. For all PO's, set $CO = SO = 0$
2. For all other nodes, set $CO = SO = \infty$
3. Propagate observability from PO's to PI's 
(note: no iteration needed for CO/SO)

Controllability Computation - 1

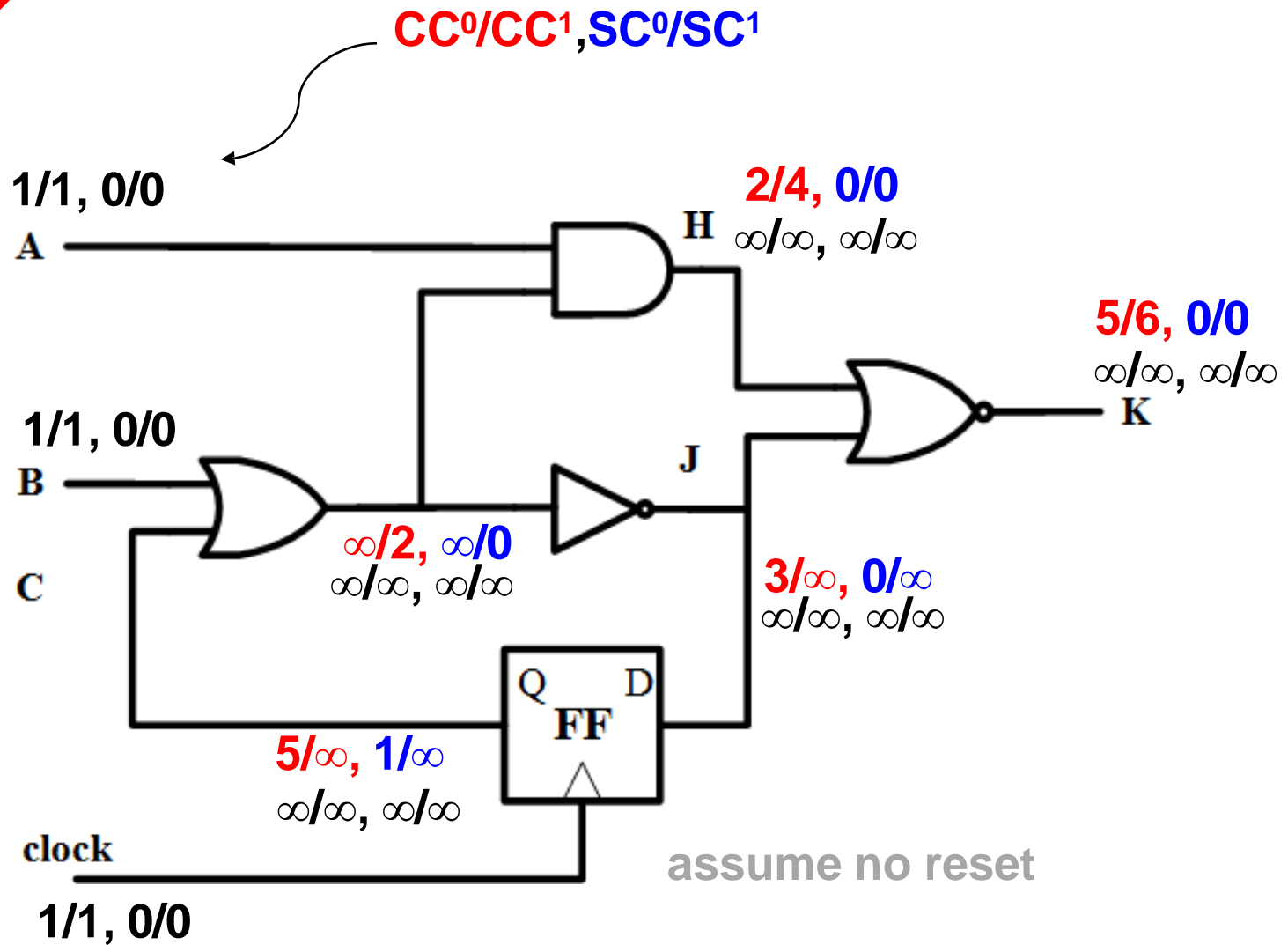
 


Quiz

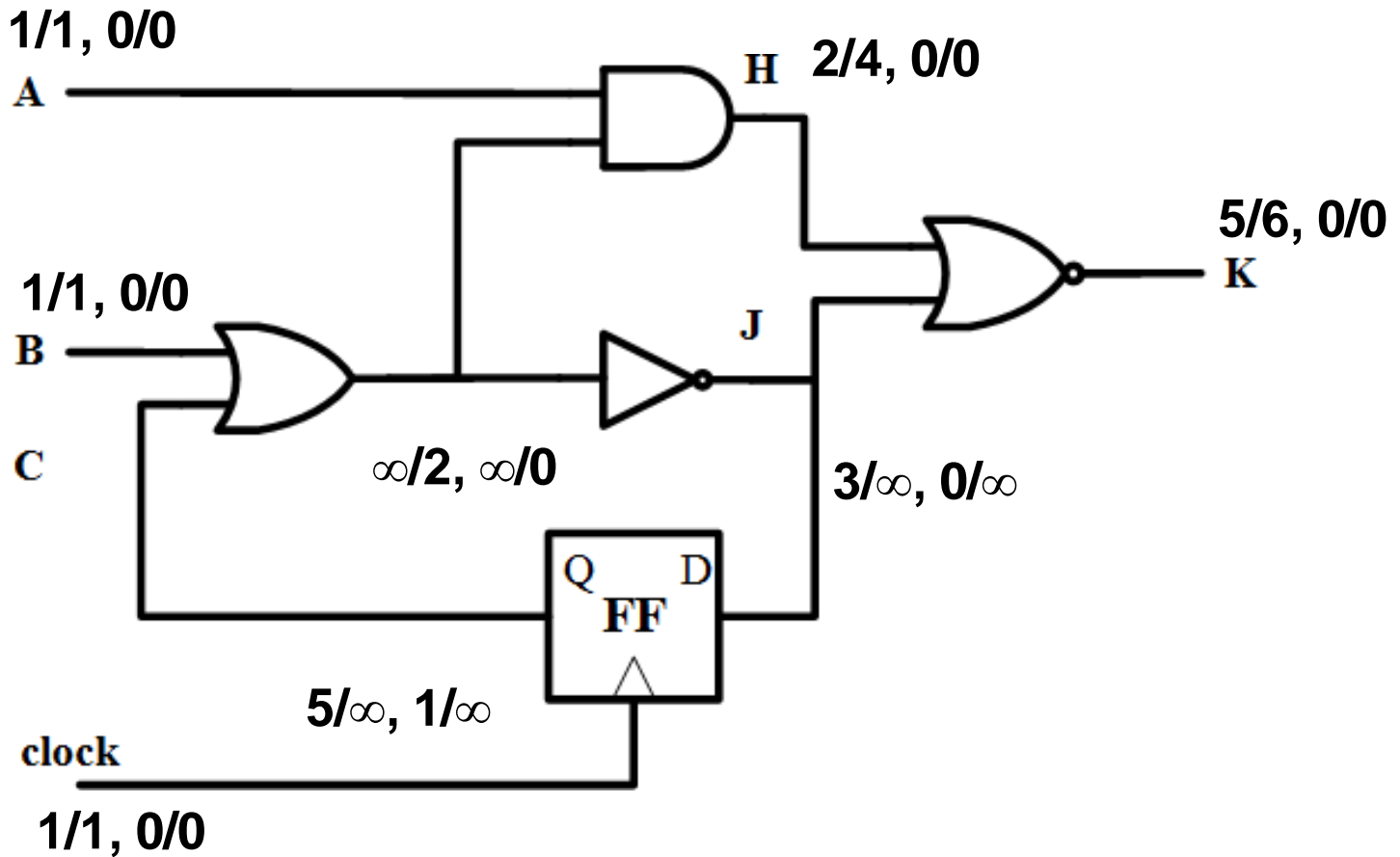
Q: Given numbers from the 1st iteration, please continue to calculate CC^0/CC^1 , SC^0/SC^1 in 2nd iteration.



Controllability Computation - 2

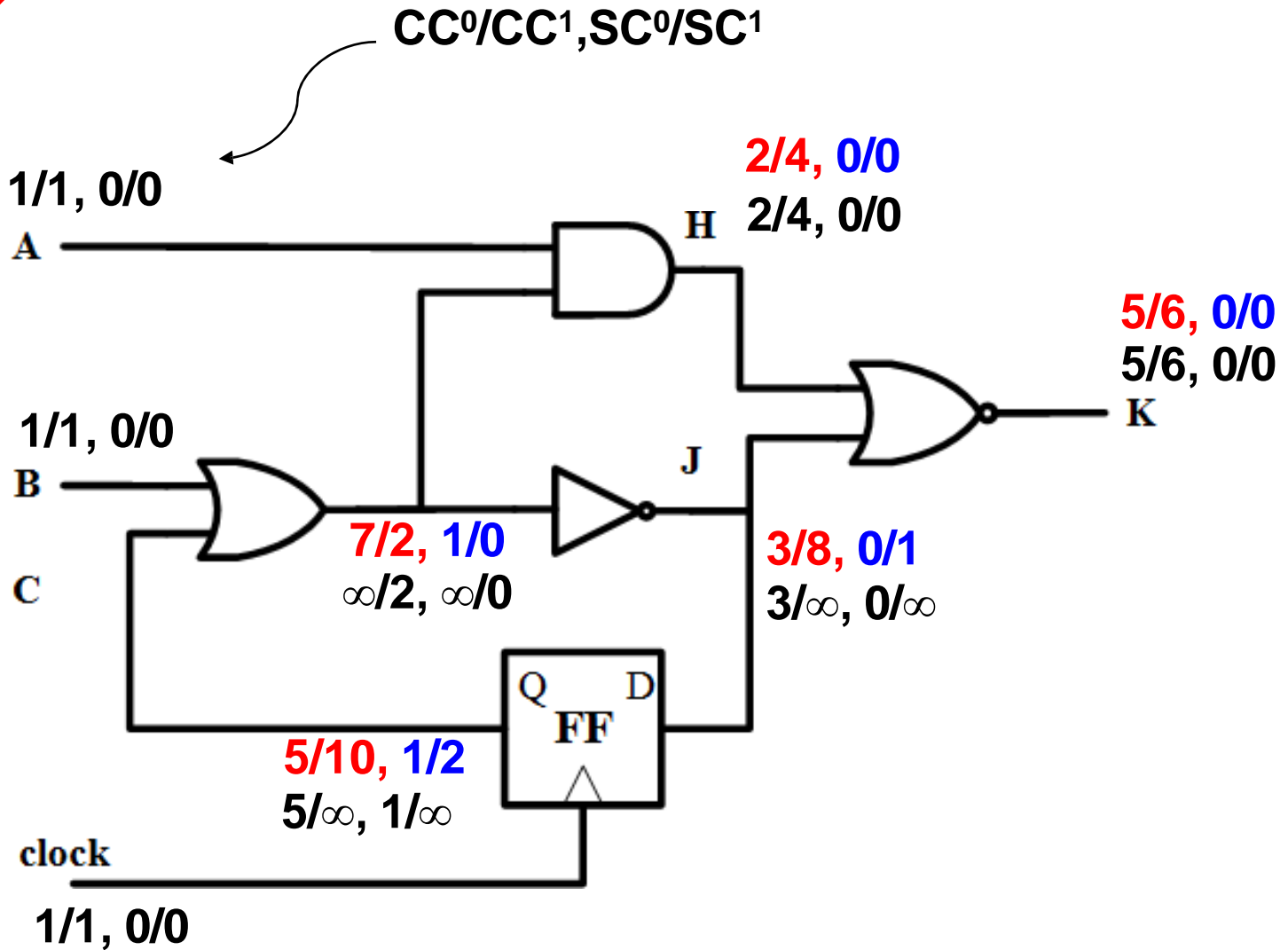 


Controllability Computation - 3

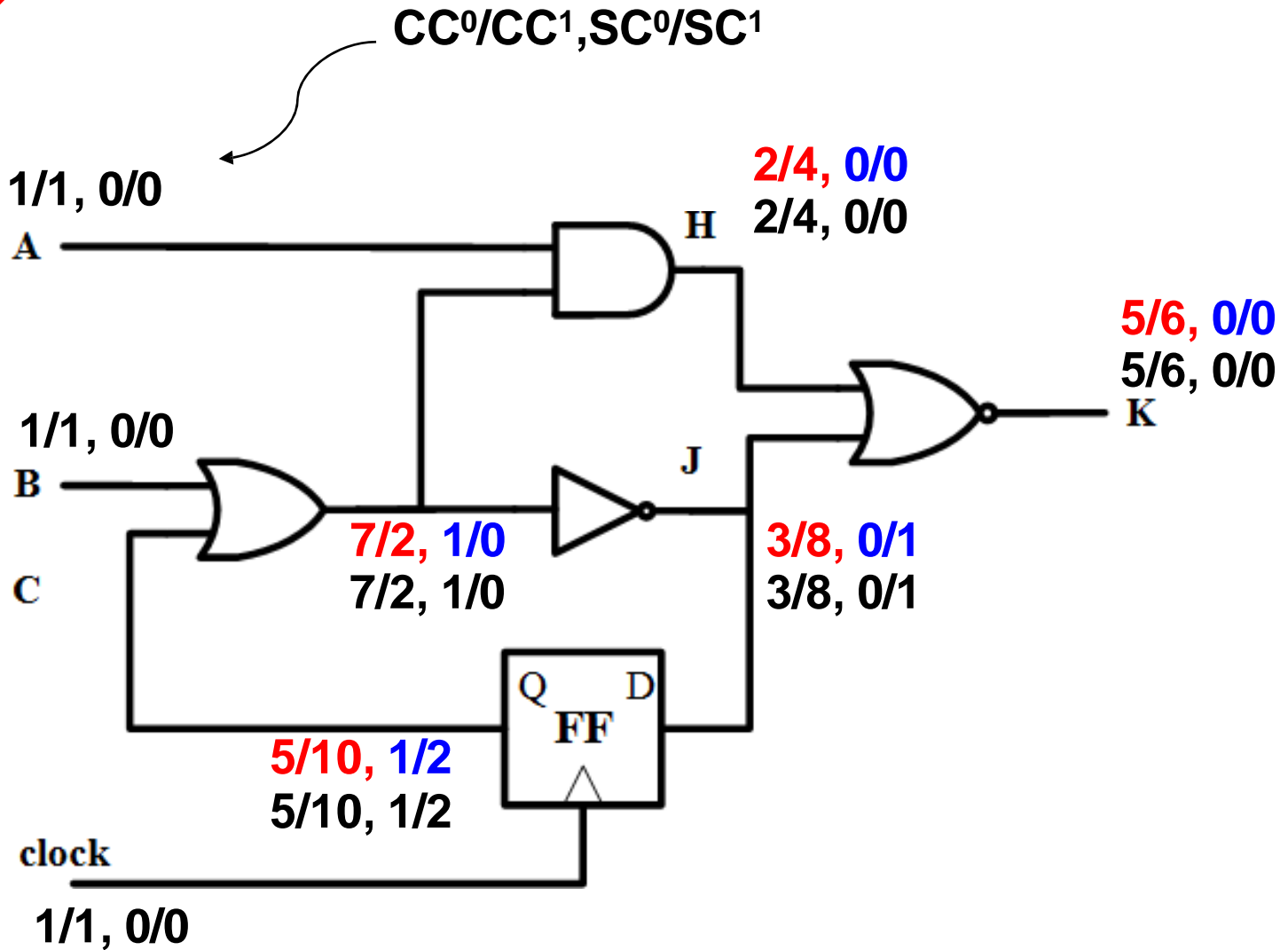


Quiz

 Q1: Generate a sequence of test patterns to control C to 0?
Q2: Generate a sequence of test patterns to control C to 1?
(assume no scan. can only assign PI)





What Does $SC^1=2$ Mean?

 - Control C to zero is easier. Assign $B=1$ and pulse **one** clock
- Control C to one is more difficult. Assign $B=1$ and $B=0$. **Two** clocks




Observability Computation

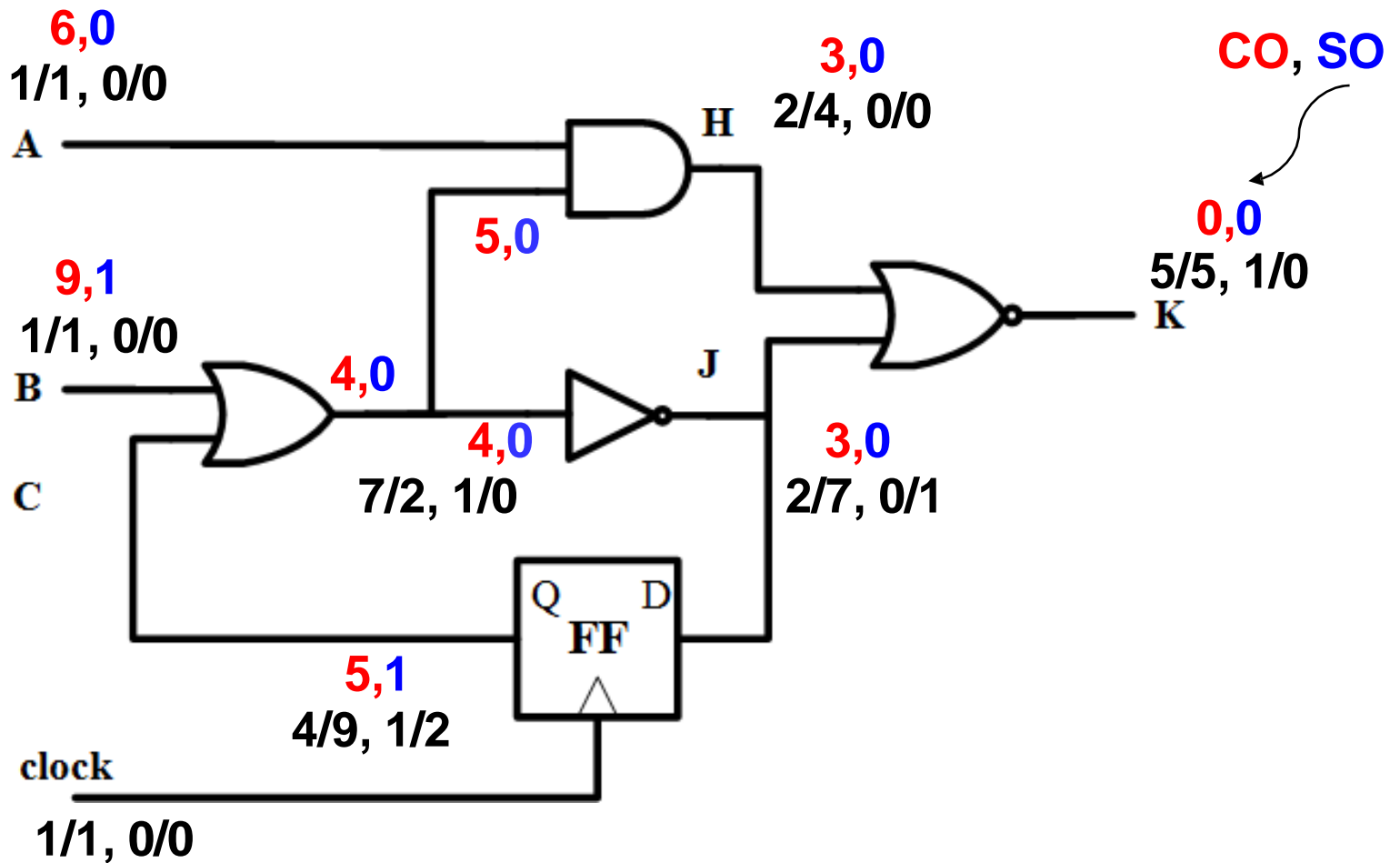 


Quiz

 Q1: Generate a sequence of test patterns to observe *A*?
Q2: Generate a sequence of test patterns to observe *B*?
(assume no scan. can only assign PI)



FFT

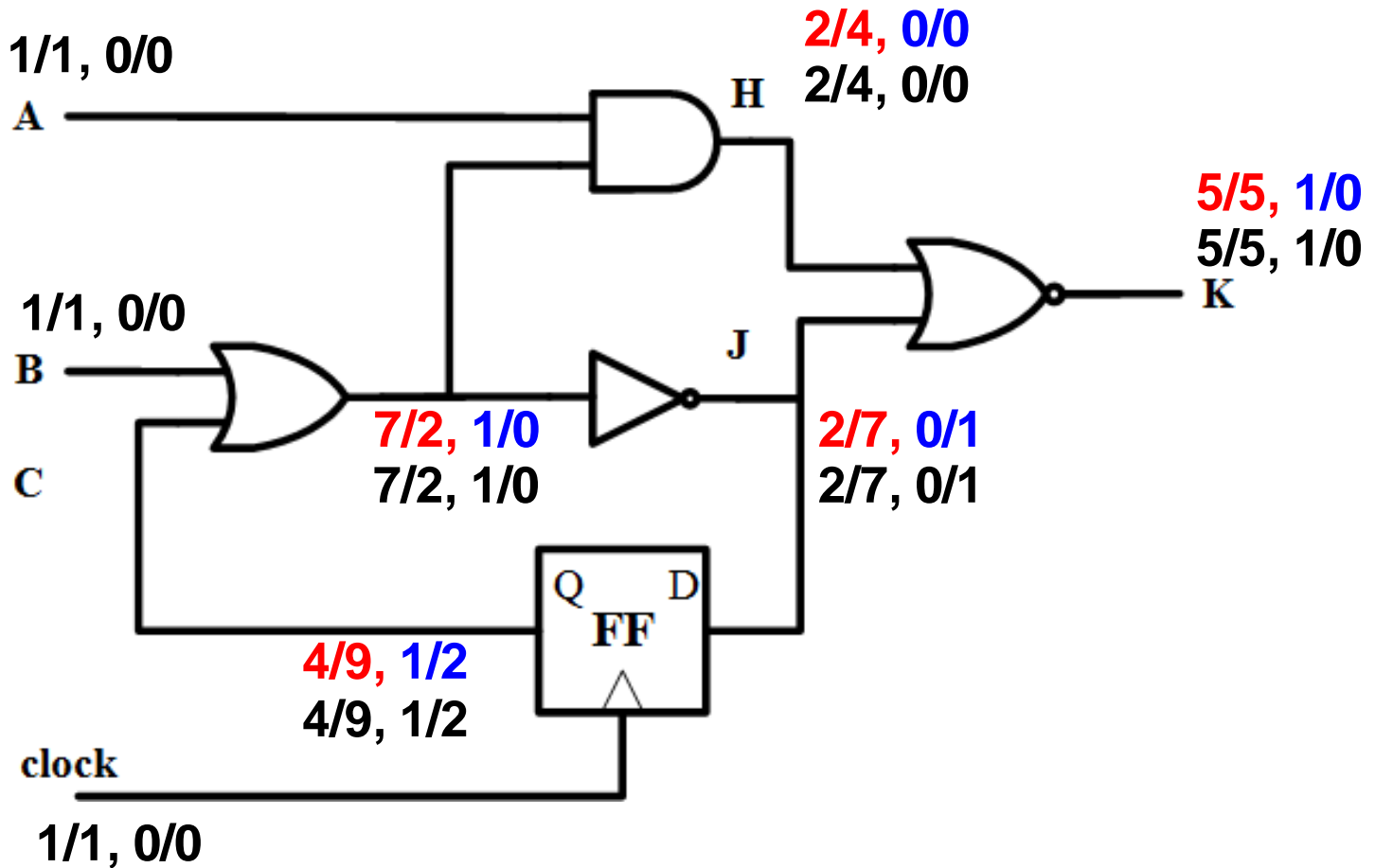- When does the algorithm fail to converge?






Computing Sequential SCOAP

- Computation of $SC^0(M)$, $SC^1(M)$, and $SO(M)$ is similar to
 - ♦ $CC^0(M)$, $CC^1(M)$, and $CO(M)$.
- Differences are
 - ① Increments sequential SCOAP by 1 only when signals propagate from **FF** inputs to Q, or backwards
 - ② May require *iterations* for controllability to converge

COP

- **Signal probability of x = probability of x being logic 1**
 - ♦ Actual signal probability requires exhaustive simulation
 - ♦ Hard to obtain in practice
- **COP = Controllability/Observability Program [Brglez 84]**
 - ♦ Fast algorithm to estimate signal probability
 - ♦ C_x = estimated $\text{prob}(x = 1)$
 - ♦ $1 - C_x$ = estimated $\text{prob}(x = 0)$
 - ♦ O_x = estimated probability of *fault effect* in x being observed at PO
- C_x and O_x are numbers between 0 and 1
 - ♦ **Larger number** means **easier** to control or observe
- Assumptions
 - ♦ 1. Ignore fanout reconvergence for fast run time
 - ♦ 2. PI are independent random numbers: $\frac{1}{2}$ zero and $\frac{1}{2}$ one


COP

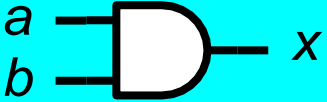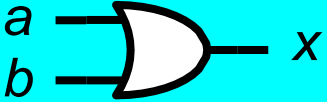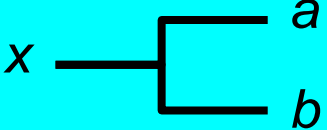	C_x	O_a
$x = \text{PI}$	0.5	
$x = \text{PO}$		0.5
	$C_x = C_a \times C_b$	$O_a = O_x \times C_b$
	$C_x = 1 - (1 - C_a) \times (1 - C_b)$	$O_a = O_x \times (1 - C_b)$
	$C_x = C_a = C_b$	$O_x = 1 - (1 - O_a) \times (1 - O_b)$


Example – Controllability

- Calculate from PI to PO
- **Fanout-free circuit**, COP = actual signal probability

COP C_x

 


Actual signal probability

 


Example (2) – Controllability

- When fanouts reconverge, COP \neq actual signal probability

COP C_x

 


Actual signal probability

 


Example (2) – Observability

- Calculate from PO to PI

COP O_x

 

COP C_x

 


Quiz

Q: verify actual signal probability by exhaustive test patterns

input	output
000	
001	
010	
011	
100	
101	
110	
111	


Actual signal probability

 


Detection Probability, DP

- DP_f = Probability of detecting a fault f
 - ♦ $DP_{NSA0} = C_N \times O_N$
 - ♦ $DP_{NSA1} = (1 - C_N) \times O_N$
- Larger DP_f means *easier* to detect fault f
- Example: $DP_{NSA0} = 1/4 \times 3/8 = 3/32$

C_x

 

O_x

 


Random Pattern Resistant Faults

- RPRF = Faults that are difficult to be tested by random patterns
 - ◆ *Low detectability*
 - ◆ aka. ***Hard-to-detect faults, difficult faults***
- Example:
 - ◆ stuck-at-0 fault at an n -input AND gate output
 - ◆ Need test pattern (1,1,1,...1)
 - ◆ Assume equal signal probability of 0.5 at each input
 - * $C_x = 0.5^n$
- Test generation for RPRF is difficult
 - ◆ Solutions:
 - * 1. Insert test points (See DFT lecture)
 - * 2. Weighted random patterns (see BIST lecture)

Summary




- COP

 - ♦ C_x = estimated prob($x = 1$)
- ♦ $1 - C_x$ = estimate prob($x = 0$)
- ♦ O_x = estimated probability of *fault effect* in x being observed
- ♦ **COP** \neq **actual signal probability** because fanout reconvergence



FFT

- Q: Why observability at PO is 0.5, not 1?

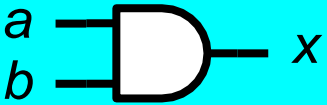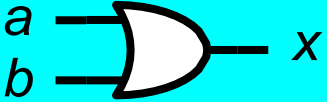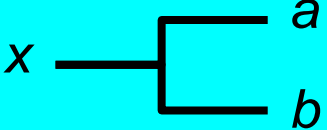	C_x	O_a
$x = PI$	0.5	
$x = PO$		0.5
	$C_x = C_a \times C_b$	$O_a = O_x \times C_b$
	$C_x = 1 - (1 - C_a) \times (1 - C_b)$	$O_a = O_x \times (1 - C_b)$
	$C_x = C_a = C_b$	$O_x = 1 - (1 - O_a) \times (1 - O_b)$