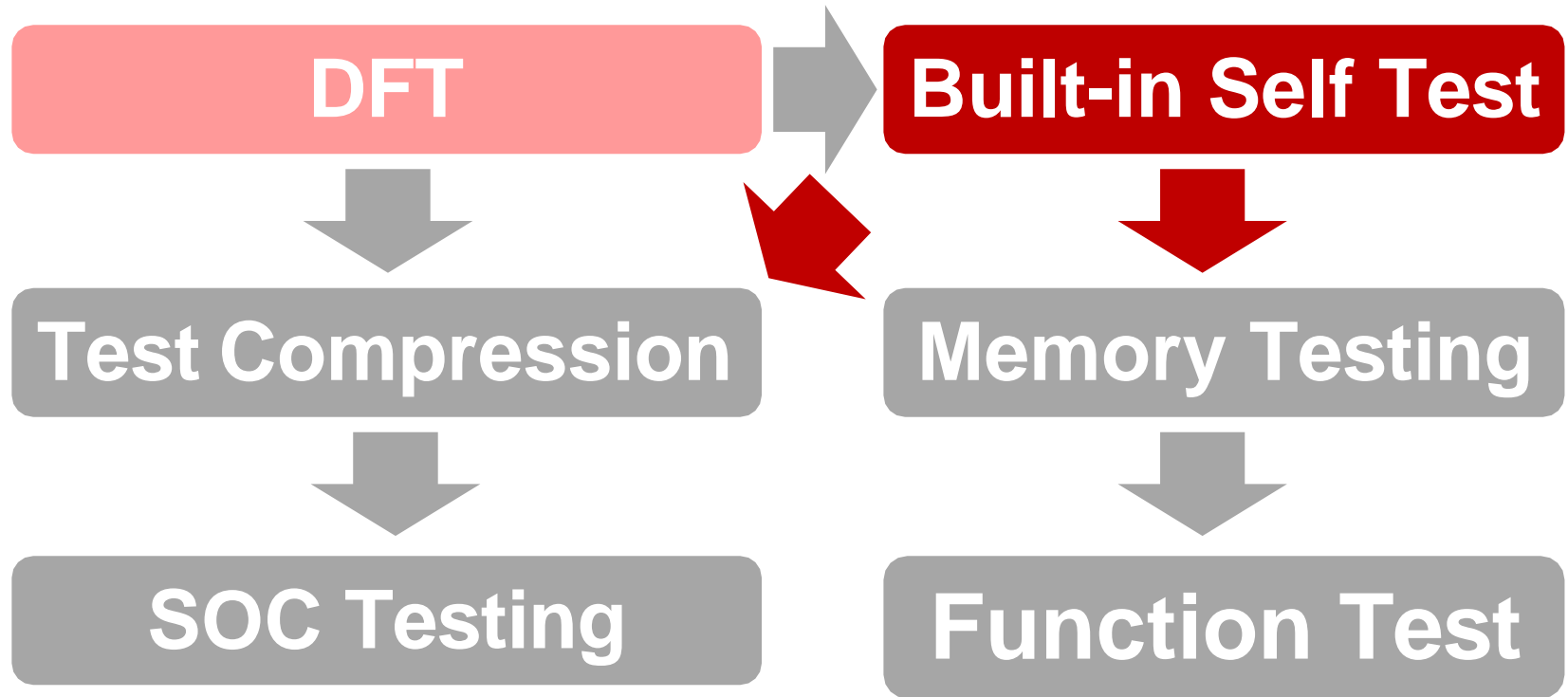



Logic Built-In Self Test (BIST)

Course Roadmap (Design Topics)



Motivating Problem

 - Your manager complains tester is too expensive.
- Please design a circuit to test the chip itself!




Why Am I Learning This?

- **Built-in Self Test (BIST) can**
 - ◆ **Remove large expensive testers**
 - ◆ **Test chips at high speed**
 - ◆ **Test chips online**

BIST Outline

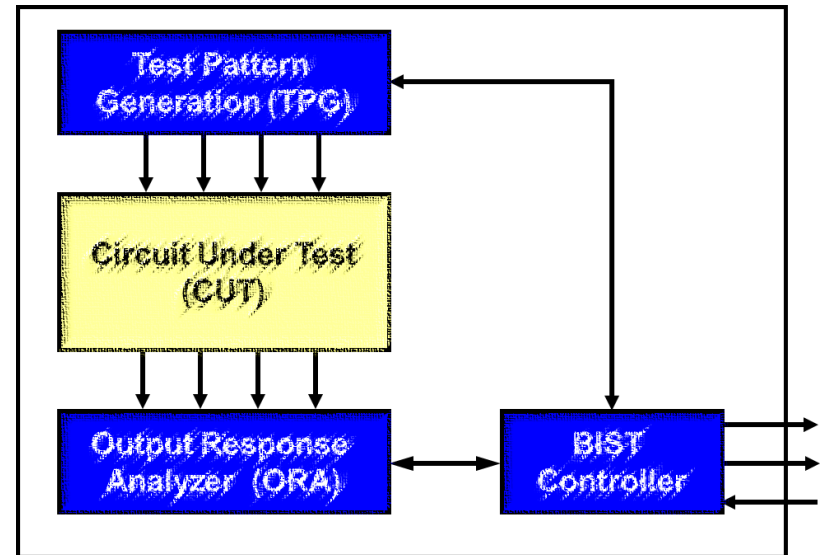- Part 1
 - ◆ Introduction
 - ◆ Test Pattern Generation
- Part 2
 - ◆ Output Response Analysis
 - ◆ BIST Architecture
 - ◆ Problems and solutions
 - ◆ Conclusions



Built-in Self Test

- Definition
 - ◆ Capability of hardware/software to carry out explicit test of itself
- Levels of BIST
 - ◆ **System-level self test**
 - * system self test of mainframe computer
 - ◆ **Board-level self test**
 - * so we can replace a bad board in a system
 - ◆ **Chip-level self test**
 - * focus of this lecture




123rf.com



IBM Blue Gene


Categories of Chip-level BIST

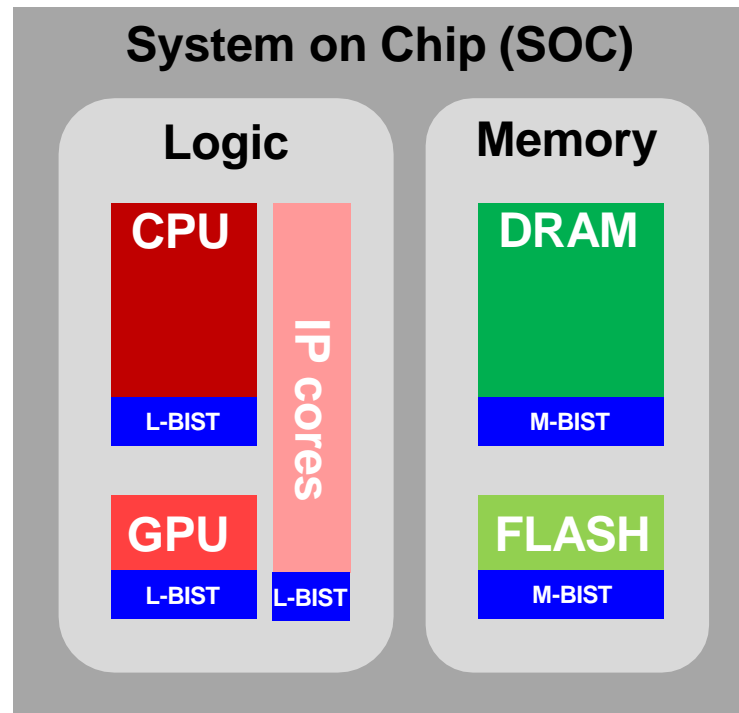- Based time of test
 - ◆ **On-line BIST**
 - * On-line testing while chip in normal operation
 - * e.g. error detection and correction for RAM
 - ◆ **Off-line BIST**
 - * Off-line testing while chip not in normal operation
 - * Focus of this talk
- Based on CUT
 - ◆ **Logic BIST**
 - ◆ **Memory BIST**




Architecture of BIST

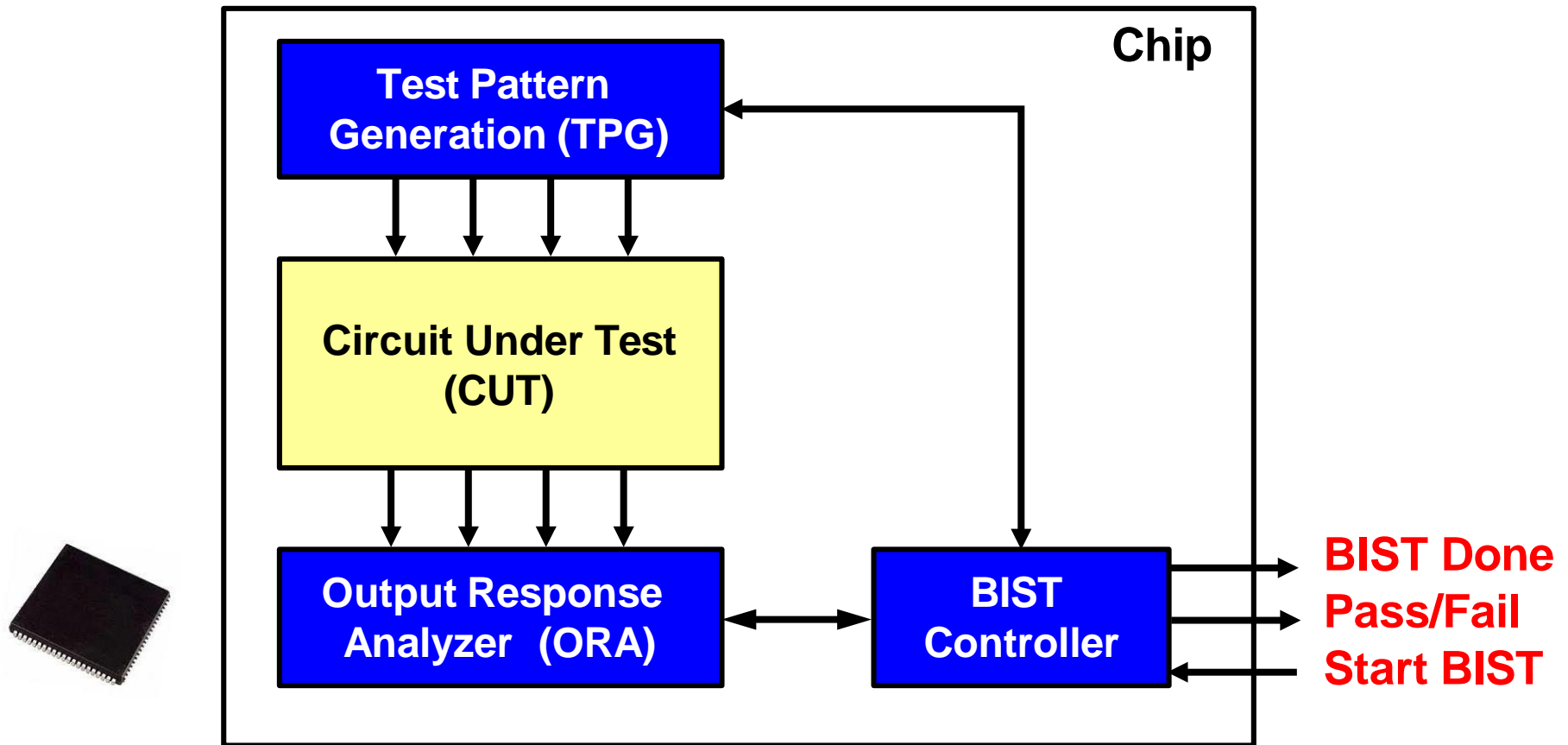- Three components: **BIST Controller, TPG, ORA**
- Three I/O Pins: **Start BIST, BIST Done, Pass/Fail**



Why BIST?

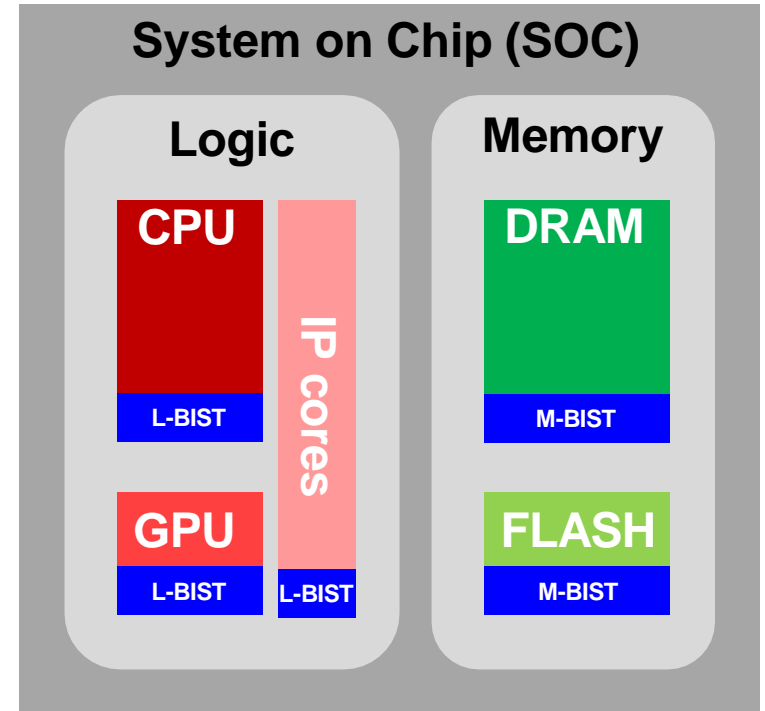- 1. Save ATE cost
 - ♦ Smaller test pattern storage
 - ♦ Fewer DFT pins
 - ♦ Slower tester speed
- 2. Better IC quality
 - ♦ Test speed higher than ATE
- 3. Easier integration of tests
 - ♦ *Intellectual Property* (IP) cores
- 4. Easier test access
 - ♦ Test embedded memory in SOC
- 5. Enable on-line testing
 - ♦ Ensure reliability



BIST Has Many Unique Advantages

ATE Cost w/wo BIST

- Consider a 1 GHz μ P with 1000 pins.
- Test w/o BIST
 - ♦ 1 GHz ATE: $\$3,000/\text{pin} \times 1,000\text{pins} = \$3,000,000 \text{ USD}$
 - ♦ Huge initial capital cost
- Test w/ BIST
 - ♦ 20 MHz ATE: $\$400/\text{pin} \times 1,000\text{pins} = \$400,000 \text{ USD}$
 - * Test I/O pad contact
 - * Provide test commands, and read out test results



BIST Reduced ATE Cost

Disadvantages of BIST

- 1. Area Overhead
 - ◆ Yield loss due to BIST circuitry
- 2. Performance degradation
 - ◆ Extra hardware
- 3. Extra design effort
 - ◆ Test point insertion, BIST insertion, verification ...
- 4. Lack information for debug and diagnosis
 - ◆ Need to bypass BIST when diagnosis
- 5. Long test length but fault coverage may not good enough
 - ◆ Random test patterns not as good as ATPG patterns
 - ◆ Mixed solution (**BIST + ATE**) is often needed

BIST can NOT Solve All Problems

Quiz


Q: Which of the following is NOT true for BIST?

- A. BIST reduces test cost because of good fault coverage**
- B. BIST reduces DFT pins required**
- C. BIST improve test quality because test speed is higher**

ANS:

BIST Part1 - TPG

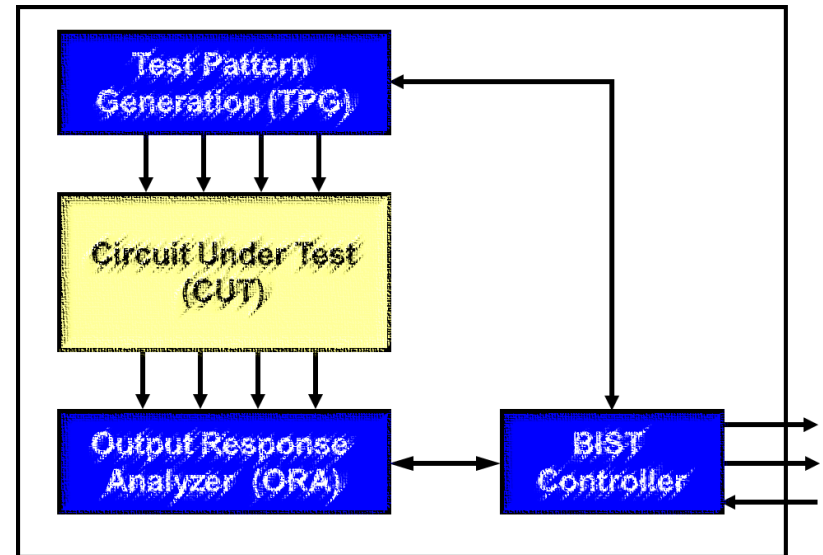
- Introduction
- Test Pattern Generation (TPG)
 - ◆ Deterministic: ROM, Algorithm, Counter
 - ◆ Pseudo Random:
 - * Linear Feedback Shift Register (LFSR)
 - * Cellular Automata (CA)



ROM/Algorithm as TPG

- **ROM as TPG**

 - ◆ Store test patterns in ROM
- ◆ Very expensive for chip-level BIST
- ◆ Maybe doable for system-level BIST
 - * e.g. self test program in BIOS (Basic Input/Output System)



- **Algorithm as TPG**

- ◆ Test pattern generation based on certain mathematical rule
- ◆ Suitable for regular structure like memory, FPGA
 - * Not very useful for random logic


No Good for Logic BIST

Shift Counters as TPG

- Generates regular test sequences
 - ♦ Such as walking sequence for interconnect testing
- Advantage: **Linear test time**
- Disadvantage: Too regular, not useful for random logic

Walking Sequence								
cycle								
1	1	0	0	0	0	0	0	0
2	0	1	0	0	0	0	0	0
3	0	0	1	0	0	0	0	0
4	0	0	0	1	0	0	0	0
5	0	0	0	0	1	0	0	0
6	0	0	0	0	0	1	0	0
7	0	0	0	0	0	0	1	0
8	0	0	0	0	0	0	0	1


line 1 2 3 4 5 6 7 8

 

← Bridging faults between lines can be detected

Binary Counters as TPG

 
- N-stage binary counters
 - ◆ Generate test patterns in sequence
 - * from 0 to 2^N-1 , or from 2^N-1 to 0
- Advantage
 - + Simple design
 - + Exhaustive test is high quality
- Disadvantages
 - Exhaustive test length is very long
 - ⇒ No randomness, deterministic pattern sequence
 - ⇒ e.g. Need 2^{N-1} test length to reach a 1 at MSB
 - Large area overhead (compared to LFSR)



Need Random Counter for Logic BIST


Summary

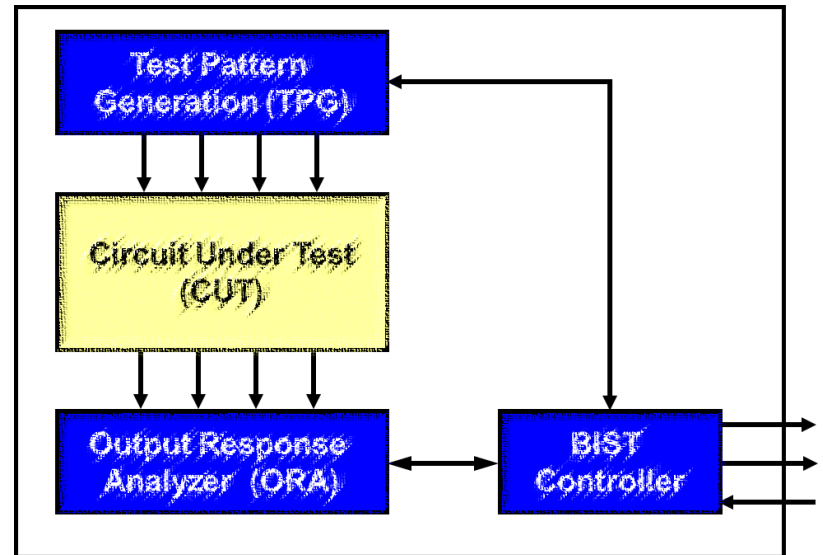- Introduction
 - ◆ BSIT components: **TPG, ORA, and controller**
 - ◆ Pros: **reduced pins, tester cost, on-line testing**
 - ◆ Cons: **area overhead, performance degradation, lower FC**
- Test Pattern Generation
 - ◆ Deterministic: **ROM, Algorithm, Counter**



BIST Part1 - TPG

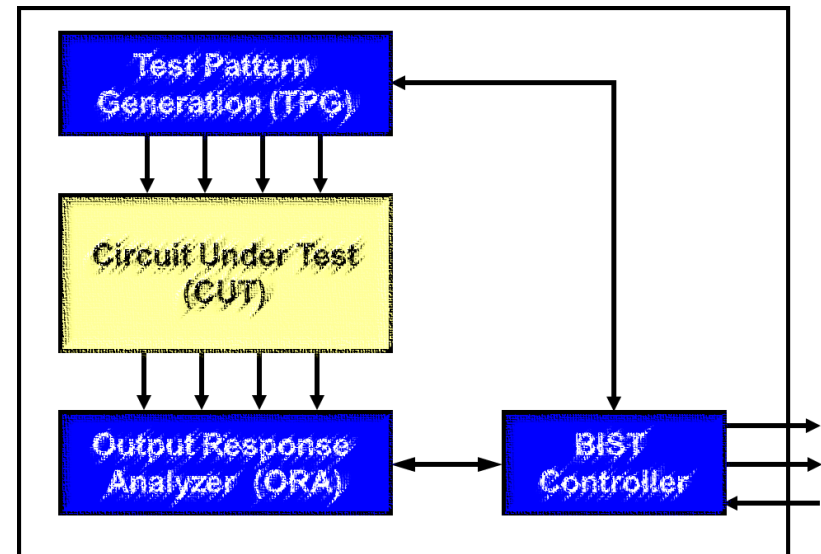- Introduction
- Test Pattern Generation (TPG)
 - ◆ Deterministic: ROM Algorithm Counter
 - ◆ Pseudo Random
 - * Linear Feedback Shift Register, LFSR (1977)
 - Two types of LFSR
 - Design of LFSR
 - * Cellular Automata, CA (1984)




Linear Feedback Shift Register [Frohwerk 77]

- LFSR consist of unit delays (flip-flops, **FF**) and feedback (**XOR**)
- Two applications of LFSR:

 
1. LFSR without external input

- * Used for **TPG**
- * aka *Autonomous LFSR*



2. LFSR with external input

- * Used for **ORA**

 


\oplus = XOR

- “Linear” because XOR is *mod-2 addition*


Two Types of Autonomous LFSR

- Autonomous LFSR is **Modular Counter**
 - ♦ Very **small area**, generate **pseudo random outputs**
- Two structures:
 - ♦ Type 1: **Standard Form** (aka **external XOR**) LFSR
 - ♦ *Type 2: Modular Form (aka **internal XOR**) LFSR*

Type-1 Standard LFSR

 

Type-2 Modular LFSR

 

LFSR is Good for TPG

Type-1, Standard Form LFSR

- Three ways to describe LFSR


1. **Next state equation:** $Q_3^+ = Q_3 \oplus Q_0$

* Q_3^+ means next state of FF Q_3

2. **Recurrence equation:** $q_m = q_{m-1} \oplus q_{m-4}$

3. **Characteristic polynomial:** $f(x) = x^4 + x^3 + 1$

* Most popular.

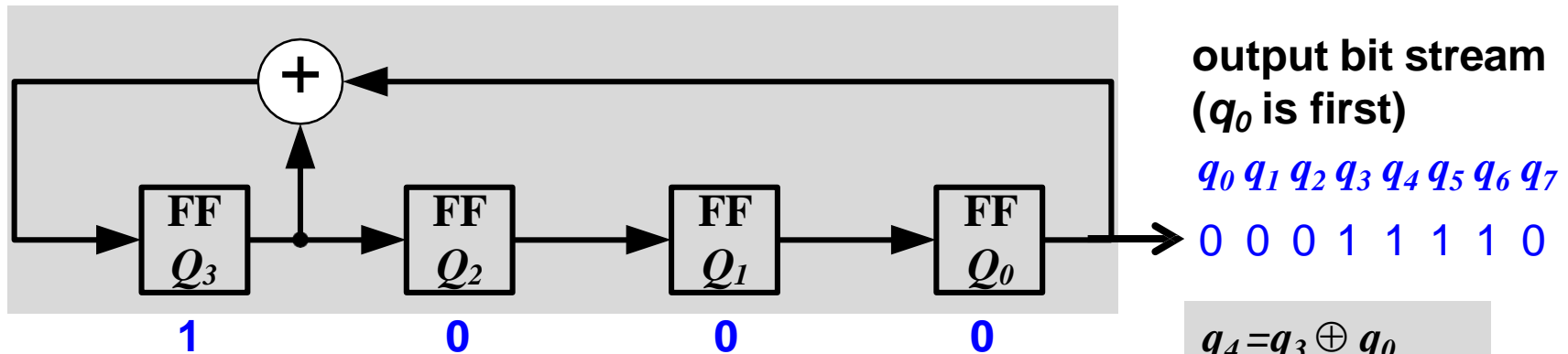


$$\begin{aligned} q_4 &= q_3 \oplus q_0 \\ q_5 &= q_4 \oplus q_1 \\ &\dots \\ q_m &= q_{m-1} \oplus q_{m-4} \end{aligned}$$

- NOTE: Modular-2 arithmetic: \oplus + - are same

♦ $1 \oplus 1 = 0$; $0 \oplus 1 = 1$; $1 \oplus 0 = 1$; $0 \oplus 0 = 0$

State Sequence of x^4+x^3+1 LFSR

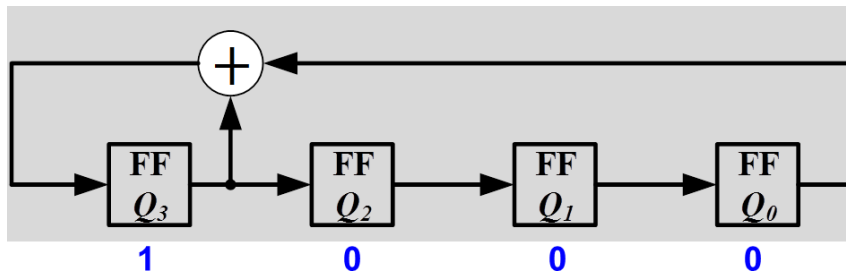- **Seed** = Initial state of LFSR
 - ♦ must be non-zero
- Total $2^4-1 = 15$ distinct states
 - ♦ All-zero state not included
- Periodical.
 - ♦ Cycle length $L_c = 15$




Back to seed after 15 cycles →


state	Q_3	Q_2	Q_1	Q_0
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	1	0	1	1
6	0	1	0	1
7	1	0	1	0
8	1	1	0	1
9	0	1	1	0
10	0	0	1	1
11	1	0	0	1
12	0	1	0	0
13	0	0	1	0
14	0	0	0	1
15 (=0)	1	0	0	0

seed

State Diagram

 


$$f(x) = x^4 + x^3 + 1$$

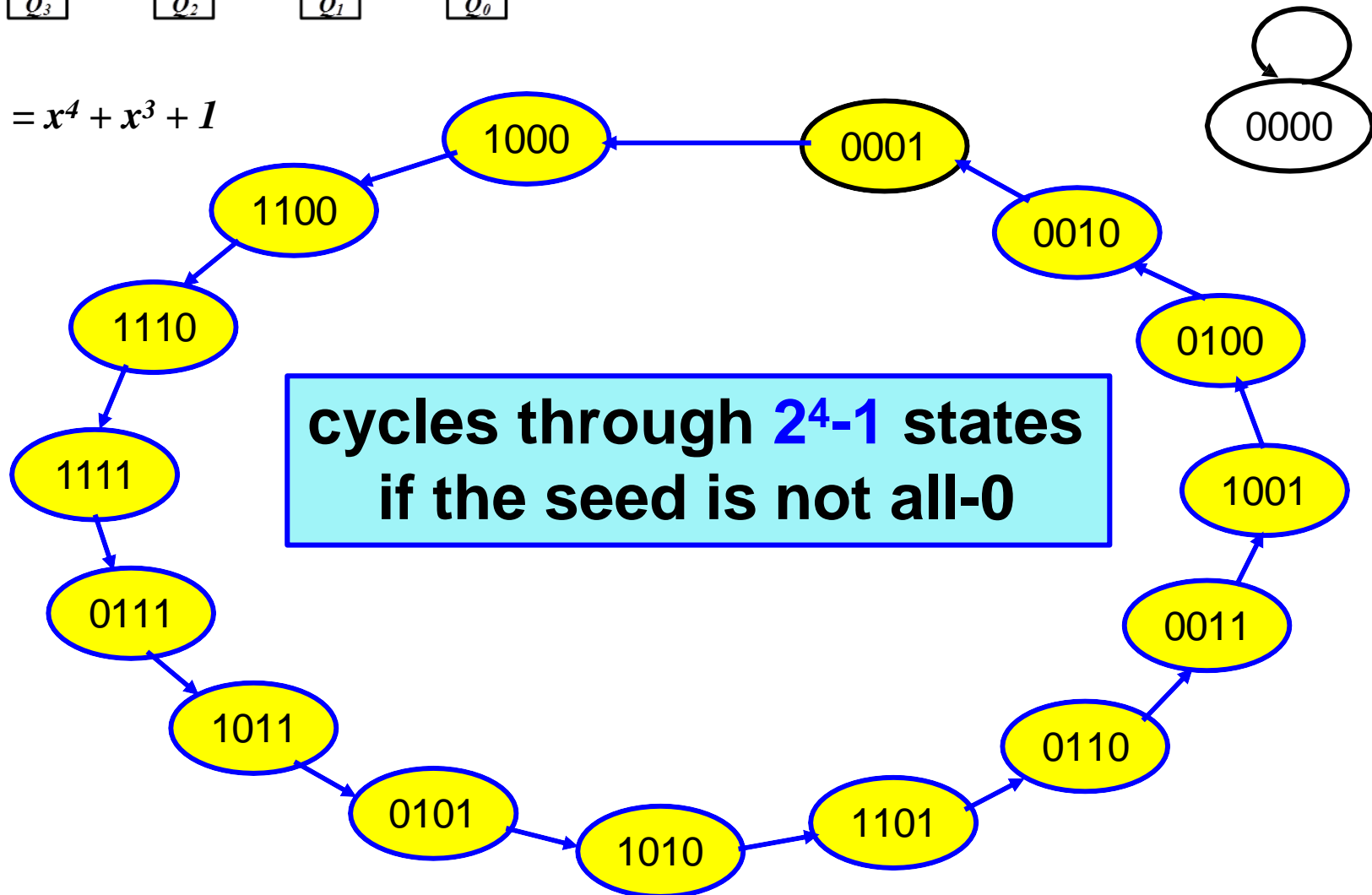

Pseudo Random Pattern Generator (PRPG)

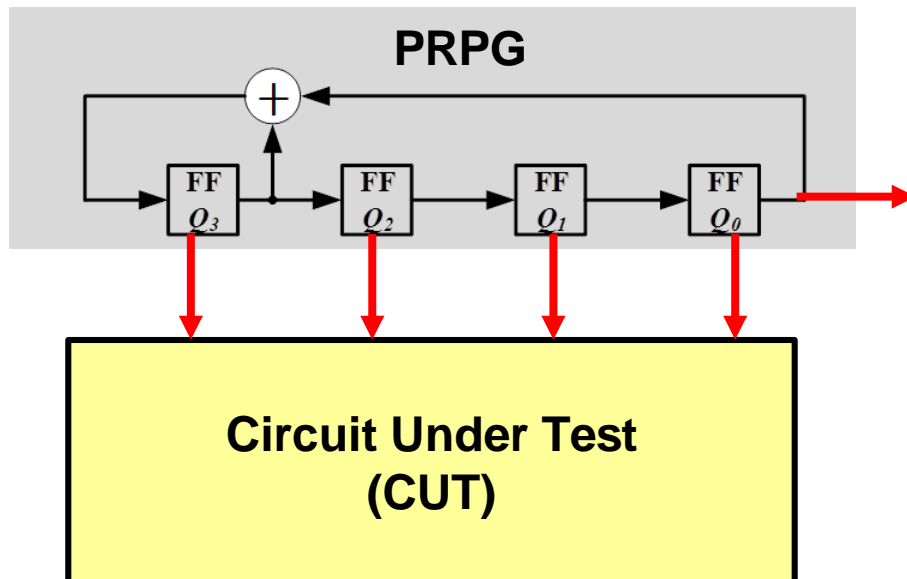- **Pseudo random.** NOT truly random
- Serial PRPG: $q_0, q_1, q_2, q_3, \dots$
 - ♦ Periodical. $L_c = 15$
- Parallel PRPG: (Q_3, Q_2, Q_1, Q_0)
 - ♦ Each output **shifted by one cycle**
 - ♦ **Phase difference** = 1




state	Q_3	Q_2	Q_1	Q_0	
0	1	0	0	0	q_0
1	1	1	0	0	q_1
2	1	1	1	0	q_2
3	1	1	1	1	q_3
4	0	1	1	1	q_4
5	1	0	1	1	q_5
6	0	1	0	1	q_6
7	1	0	1	0	q_7
8	1	1	0	1	q_8
9	0	1	1	0	q_9
10	0	0	1	1	q_{10}
11	1	0	0	1	q_{11}
12	0	1	0	0	q_{12}
13	0	0	1	0	q_{13}
14	0	0	0	1	q_{14}
15 (=0)	1	0	0	0	q_{15}

Phase diff. = 1

Quiz

Q: Given this new LFSR, show the state sequences with seed [1 0 0 0]


Q2: What is cycle length L_c ?

 

state	Q_3	Q_2	Q_1	Q_0
0	1	0	0	0
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				
13				
14				
15				

N-degree Standard Form LFSR

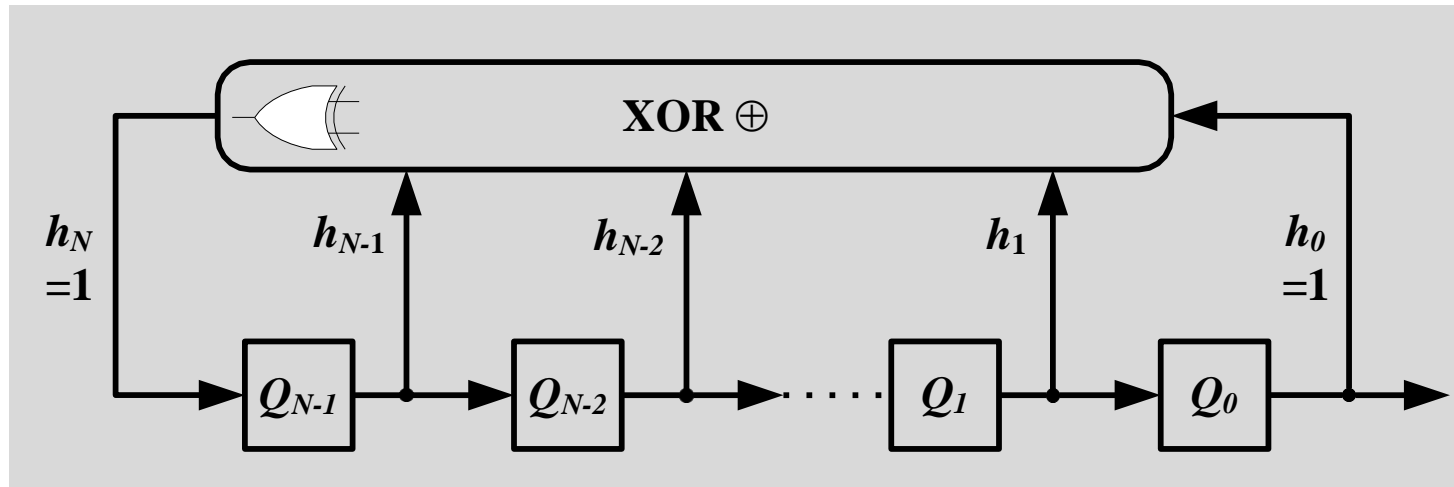
- **$N = \text{LFSR degree} = \text{number of FF} = \text{characteristic polynomial degree}$**



$h_i = 1$ if feedback exists

$h_i = 0$ if no feedback

$h_N = 1, h_0 = 1$

 

$$f(x) = x^4 + x^3 + 1$$

- **Characteristic polynomial:**
(details see appendix)

$$f(x) = \sum_{i=0}^N h_i x^i$$

$f(x)$ Can Be Written from LFSR Structure

Matrix Representation (Type-1 LFSR)

$$\begin{bmatrix} Q_0^+ \\ Q_1^+ \\ \vdots \\ Q_{N-3}^+ \\ Q_{N-2}^+ \\ Q_{N-1}^+ \end{bmatrix} = \begin{bmatrix} \begin{matrix} 0 & 1 & 0 & \dots & 0 & 0 \\ 0 & 0 & 1 & \dots & 0 & 0 \\ \vdots & 0 & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 1 & 0 \\ 0 & 0 & 0 & \dots & 0 & 1 \end{matrix} \\ \begin{matrix} h_0 & h_1 & h_2 & \dots & h_{N-2} & h_{N-1} \end{matrix} \end{bmatrix} \begin{bmatrix} Q_0 \\ Q_1 \\ \vdots \\ Q_{N-3} \\ Q_{N-2} \\ Q_{N-1} \end{bmatrix}$$


Identity matrix

$$Q^+ = T Q \pmod{2}$$


Q = current state

Q^+ = next state

T = *companion matrix*

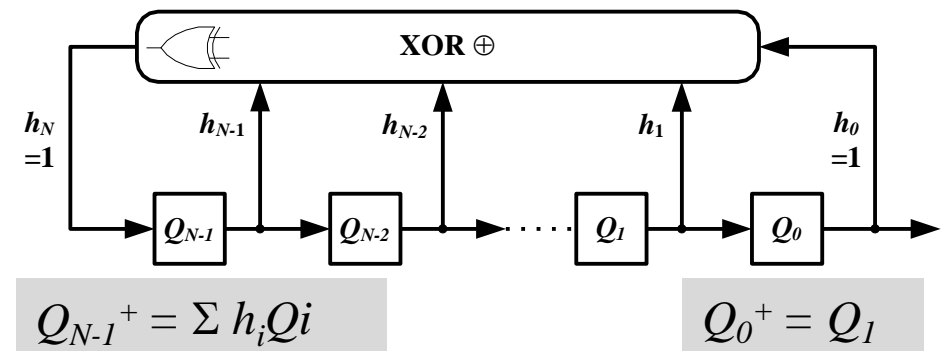

Example

 

state	Q ₃	Q ₂	Q ₁	Q ₀
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1

$$T = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \end{bmatrix}$$

$$T^2 = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix}$$

mod-2 arithmetic:
 $1 \times 1 = 1$ $1 \times 0 = 0$ $0 \times 0 = 0$
 $1 + 1 = 0$ $1 + 0 = 1$ $0 + 0 = 0$

$$Q_{seed} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix}$$

$$TQ_{seed} = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 1 \\ 1 \end{bmatrix}$$


$$T^2Q_{seed} = \begin{bmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 1 \\ 1 \end{bmatrix}$$

$$T^3Q_{seed} = T^2TQ_{seed} = \begin{bmatrix} 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \\ 1 & 1 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix}$$

**Matrix Multiplication
Same as Simulation**

Linear Relationship between States

 - 0th cycle: LFSR state = Q_{seed}
- 1st cycle: TQ_{seed}
- 2nd cycle: $TTQ_{seed} = T^2Q_{seed}$
- 4th cycle: $T^4Q_{seed} = (T^2)^2Q_{seed}$
- 16th cycle: $T^{16}Q_{seed} = (T^8)^2Q_{seed} = (((T^2)^2)^2)^2Q_{seed}$
 - ♦ only 4 matrix squares needed
- After L_c cycles, LFSR returns to initial state
 - ♦ $T^{L_c}Q_{seed} = Q_{seed}$
 - ♦ In this case $L_c=15$. $T^{15} = I$, so $T^{16} = T$




Matrix Faster Than Simulation

Quiz

Q1: Given this LFSR, What is its characteristic polynomial?

Q2: What is its companion matrix T ?

 Q3: Use T to derive state after three cycles, starting from seed $[1\ 0\ 0\ 0]$




state	Q_3	Q_2	Q_1	Q_0
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	1	0	0	1

ANS


LFSR Types

- *Type 1: Standard Form (aka external XOR) LFSR*
- *Type 2: **Modular Form** (aka **internal XOR**) LFSR*
 - ♦ XOR gates are **internal** to LFSR
 - ♦ as opposed to standard form LFSR, in which XOR are **external**

Type-1 Standard LFSR

 


Type-2 Modular LFSR

 

NOTE: Order of FF Different

N-degree Modular Form LFSR

 - $N = \text{LFSR degree} = \text{number of FF} = \text{characteristic polynomial degree}$




$h_i = 1$ if feedback exists

$h_i = 0$ if no feedback

$h_N = 1, h_0 = 1$

- Characteristic polynomial:**

$$f(x) = \sum_{i=0}^N h_i x^i$$

 

$$f(x) = x^4 + x^3 + 1$$

$f(x)$ Same as Type-1 LFSR
(remember correct order of FF !)

Matrix Representation (Type-2 LFSR)

$$\begin{bmatrix} Q_0^+ \\ Q_1^+ \\ \vdots \\ \vdots \\ Q_{N-3}^+ \\ Q_{N-2}^+ \\ Q_{N-1}^+ \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & \dots & 0 \\ 1 & 0 & 0 & \dots & 0 \\ \vdots & 1 & \vdots & \dots & \vdots \\ \vdots & \vdots & \vdots & \dots & \vdots \\ 0 & 0 & 1 & \dots & 0 \\ 0 & 0 & 0 & \dots & 0 \\ 0 & 0 & 0 & \dots & 1 \end{bmatrix} \begin{bmatrix} h_0 \\ h_1 \\ h_2 \\ \vdots \\ h_{N-2} \\ h_{N-1} \end{bmatrix} \begin{bmatrix} Q_0 \\ Q_1 \\ \vdots \\ \vdots \\ Q_{N-3} \\ Q_{N-2} \\ Q_{N-1} \end{bmatrix}$$


Identity matrix

$$Q^+ = T Q$$

Q = current state


Q^+ = next state

T = Companion matrix

 


Quiz

 Q: Given two types LFSR of x^4+x^3+1 , same seed 1000, fill in table.



state	Q_3	Q_2	Q_1	Q_0
0	1	0	0	0
1	1	1	0	0
2	1	1	1	0
3	1	1	1	1
4	0	1	1	1
5	1	0	1	1
6	0	1	0	1
7	1	0	1	0
8	1	1	0	1
9	0	1	1	0
10	0	0	1	1
11	1	0	0	1
12	0	1	0	0
13	0	0	1	0
14	0	0	0	1
15 (=0)	1	0	0	0

 

state	Q ₀	Q ₁	Q ₂	Q ₃
0	1	0	0	0
1	1			
2	1			
3	1			
4	1	1		
5	1	1	1	
6	1	1	1	1
7	1	1	1	
8	1		1	1
9	1	1		
10	1		1	
11	1	1		1
12	1	1		
13	1		1	
14	1			1
15 (=0)	1			

Summary – LFSR

- Two types of LFSR. Simple structure, good for TPG
- LFSR generate pseudo random test patterns. Repeat every L_c cycles
- Linear relationship between states: $Q^+ = TQ$
- Characteristic polynomial is often used to describe LFSR

	Structure	Matrix
type1 standard-form	<p>index right to left</p>	$\begin{bmatrix} Q_0^+ \\ Q_1^+ \\ \vdots \\ Q_{N-3}^+ \\ Q_{N-2}^+ \\ Q_{N-1}^+ \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 & 0 \\ 0 & 0 & 1 & \dots & 0 & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 1 & 0 \\ 0 & 0 & 0 & \dots & 0 & 1 \\ h_0 & h_1 & h_2 & \dots & h_{N-2} & h_{N-1} \end{bmatrix} \begin{bmatrix} Q_0 \\ Q_1 \\ \vdots \\ Q_{N-3} \\ Q_{N-2} \\ Q_{N-1} \end{bmatrix}$
type2 modular-form	<p>index left to right</p>	$\begin{bmatrix} Q_0^+ \\ Q_1^+ \\ \vdots \\ Q_{N-3}^+ \\ Q_{N-2}^+ \\ Q_{N-1}^+ \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & \dots & 0 & h_0 \\ 1 & 0 & 0 & \dots & 0 & h_1 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & 1 & \dots & 0 & \vdots \\ 0 & 0 & 0 & \dots & 0 & h_{N-2} \\ 0 & 0 & 0 & \dots & 1 & h_{N-1} \end{bmatrix} \begin{bmatrix} Q_0 \\ Q_1 \\ \vdots \\ Q_{N-3} \\ Q_{N-2} \\ Q_{N-1} \end{bmatrix}$
Char. Poly	$f(x) = \sum_{i=0}^N h_i x^i$	$f(\lambda) = \det(T - \lambda I)$

Reference

- (BMS 87) P.H. Bardell, W.H. McAnney, J. Savior, *Built-in Test for VLSI: Pseudorandom Techniques*, Wiley Interscience, 1987.
- [Könemann 91] B Könemann, “LFSR-coded test patterns for scan designs,” European Test Conference, 1991