 


Design For Testability (DFT)

Part I: Internal Scan Chains

Motivating Problem

- Sequential ATPG fails to generate test pattern. Your manager asked you to **add circuits** so that this fault can be detected.
- Can we change FF to improve controllability/observability?




Design for Testability (DFT)

- What is DFT?
 - ◆ Insert circuitry that has little to do with function, but
 - ◆ Improves **testability** : controllability and observability
- Why DFT?
 - ◆ 1. Reduce **ATPG effort**
 - * Shorten ATPG run time
 - ◆ 2. Improve **test quality**
 - * High fault coverage
 - ◆ 3. Reduce **test cost**
 - * Shorten test length and test time
 - ◆ 4. Reduce **time to market**
 - * Easy debug and diagnosis



Penalty of DFT

 - 1. **Design effort overhead**
- 2. **Performance degradation**
- 3. **Hardware overhead**
 - ♦ extra area, extra pins
- 4. **Yield loss**
 - ♦ Larger area means lower yield
- 5. **Power overhead**
 - ♦ “Power tax” of testing
- In 1970's, expensive silicon and simple design, DFT not popular
 - ♦ Now, cheaper silicon and complex design, DFT is necessary



DFT is Necessary for Modern Designs

Quiz

Q: Which of the following is NOT true about DFT?

- A. DFT reduces designers' effort**
- B. DFT cost extra hardware and power**
- C. DFT reduces test cost so it is needed for complex design**


ANS:

Ad Hoc DFT

- What is “Ad hoc” ?
 - ◆ for the particular end or case at hand without consideration of wider application
- What is *Ad Hoc DFT* ?
 - ◆ DFT technique for a particular design
 - * Not generally applicable to all designs
 - ◆ Relies on **good design practice** learned from **experience**
- Ad-hoc DFT examples:
 - ◆ Rule1: design circuits easily initializable
 - ◆ Rule2: disable internal clocks during test
 - ◆ Rule3: partition large circuits into small blocks
 - ◆ Rule4: insert test points into circuits of low testability
 - ◆

Ad Hoc DFT Example (1)

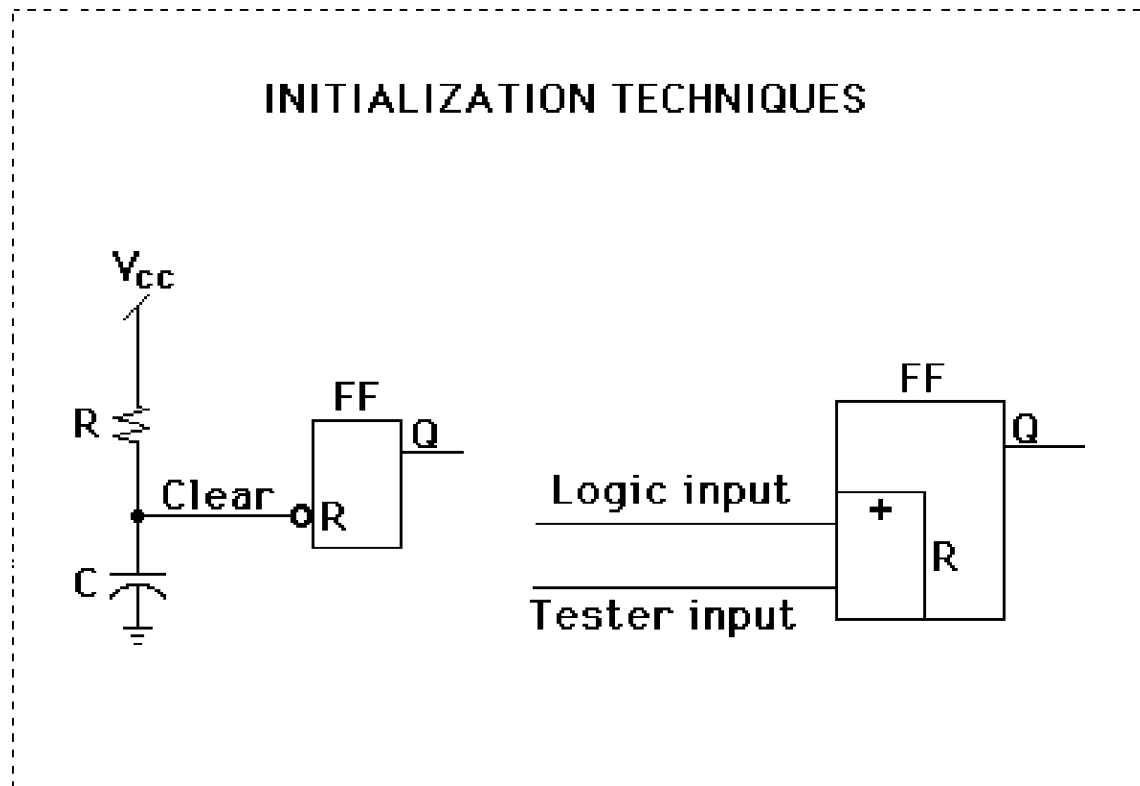
- Rule1: design circuits easily initializable
 - ◆ Self-initialization, or
 - ◆ Initializable from tester



Courtesy Prof. McClueksy, Stanford University

Ad Hoc DFT Example (2)

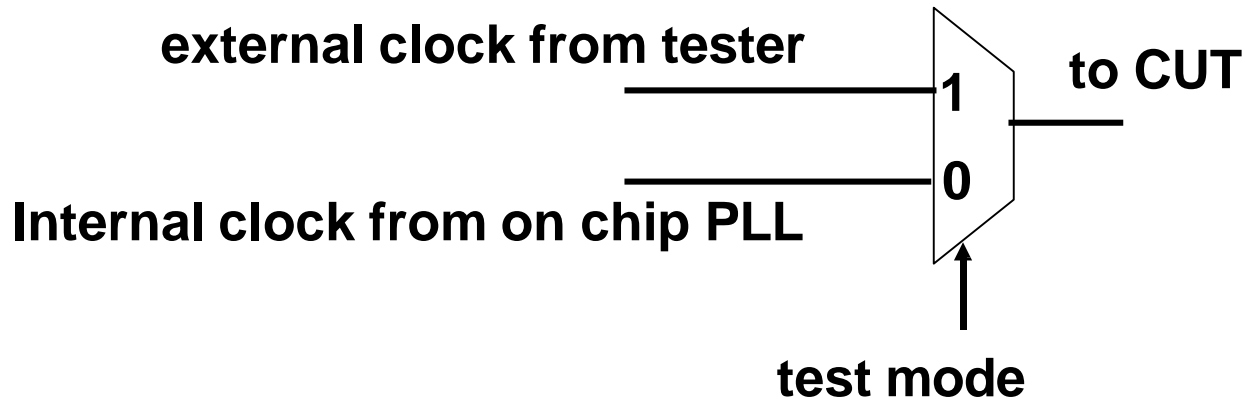- Rule2: disable internal clocks during test
 - ◆ Disable on-chip PLL in test mode



Test Point Insertion




- Objective:
 - ◆ Insert test points to enhance
 - * Controllability
 - * Observability
- Two types of test points
 - ◆ *Control points*: enhance controllability.
 - ◆ *Observation points*: enhance observability

Control Points




- Control signals come from primary input (PI) or scan FF
 - Details see next video

original




x

   

control x to 0

   


control x to 1

   

Control Point (2)

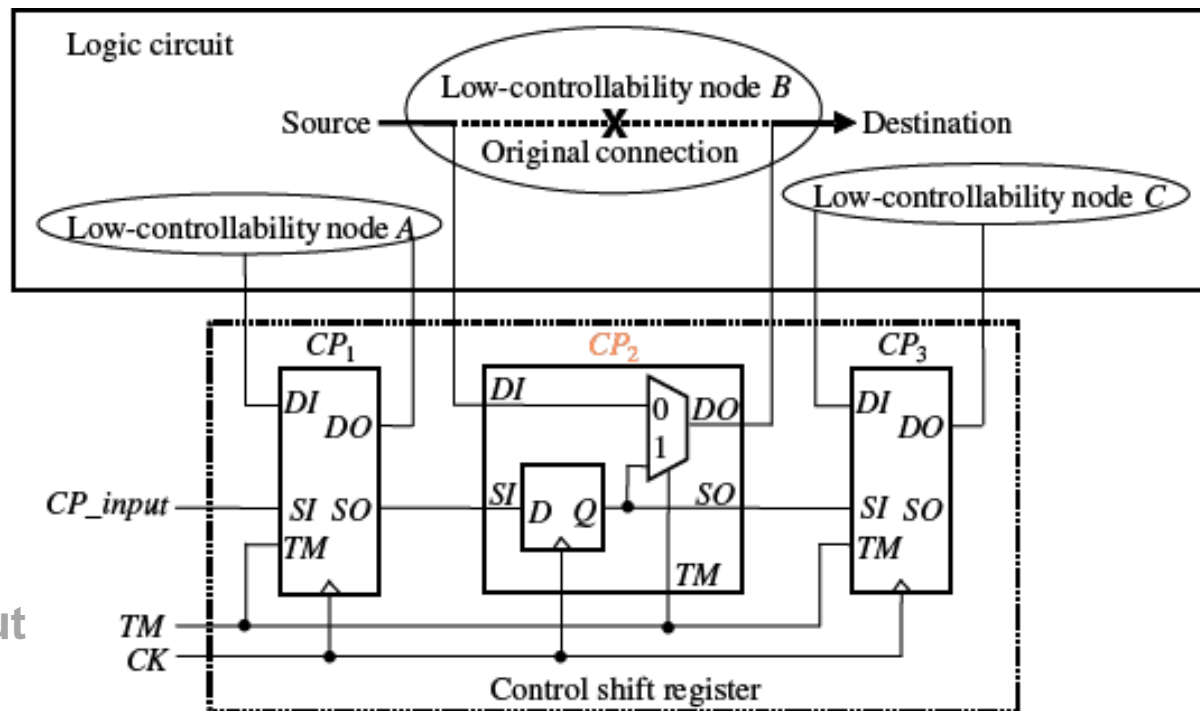- When **TM=0**, normal operation
- When **TM=1**, nodes ABC are controlled by FF 1, 2, 3, respectively



DI=data input
DO=data output
TM=test mode
SI=scan input
SO=scan output




Control point insertion

Quiz




Q: What are control values in NORMAL mode?

ANS:

Test mode

   


Normal mode

   

Observation Points

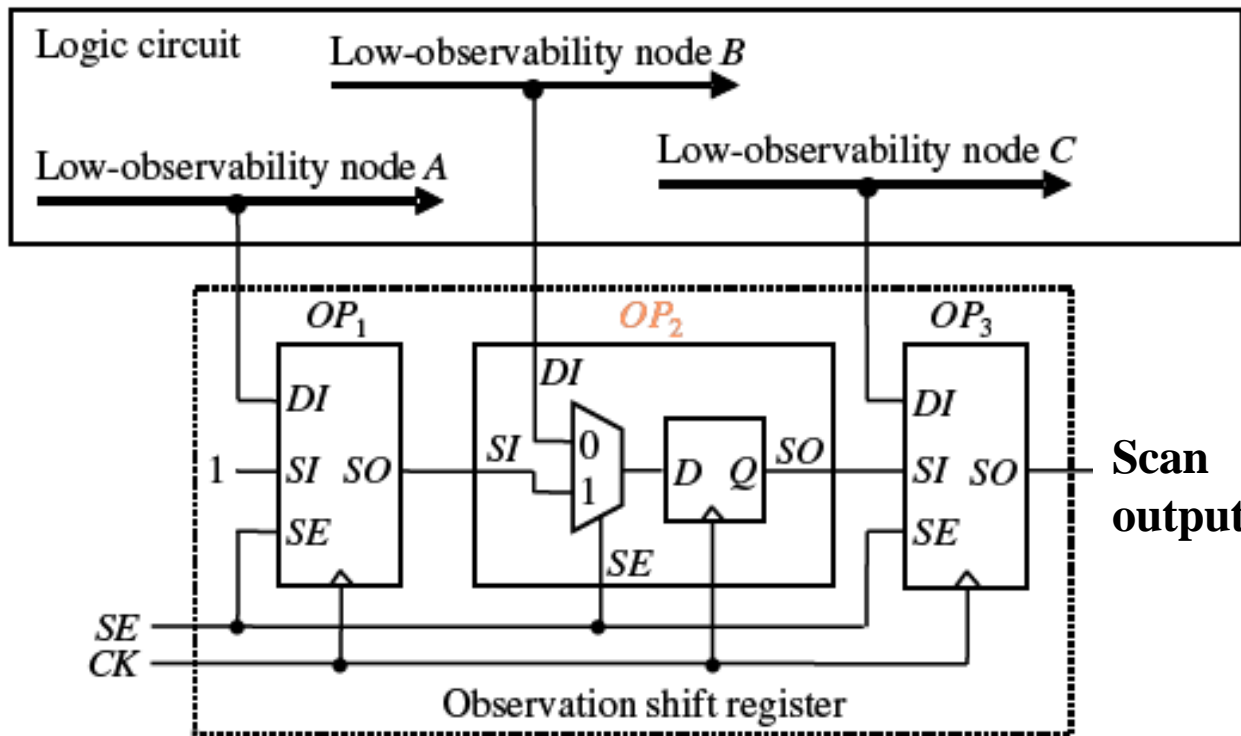- **SE=0**, ABC are captured into FF by one CK
- **SE=1**, after three CK, values are observed at scan output (SO)




DI=date input
DO=data output
SE=scan enable
SI=scan input
SO=scan output

Observation point insertion

Issues with Test Points

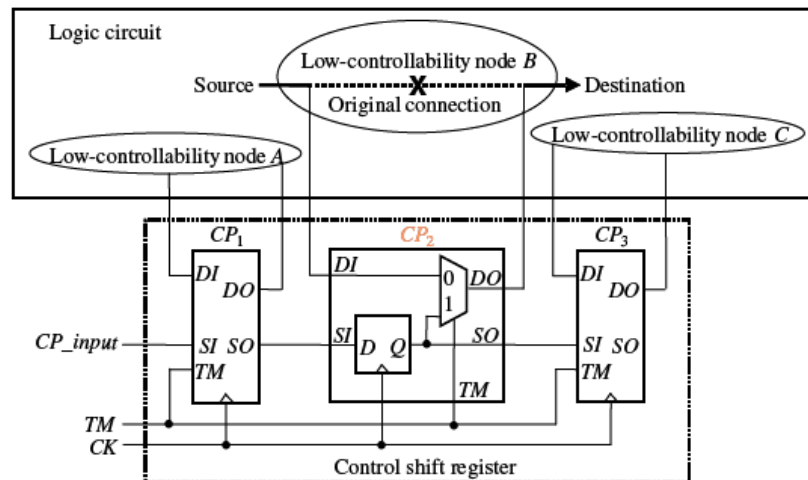- 1. Performance degradation
 - ♦ design slower with test points
- 2. Area overhead
 - ♦ About 1 test point every 1K gates
- 3. Pin overhead
- 4. Where to insert test points?
 - ♦ Need testability measure
- 5. Built-in Self Test (BIST) needs test point more than ATPG
 - ♦ Improve fault coverage , see BIST chapter



Summary



- Introduction to DFT
 - ◆ DFT helps to improve **controllability/observability**
 - ◆ **Ad-hoc DFT** based on experience
 - * Advantage
 - Suitable for your particular design under test
 - * Disadvantage
 - Not systematic → **lacks EDA tool**
 - As opposed to **structured DFT**
 - ◆ Test point insertion
 - * control point/ observation points
 - * **EDA tools ready** for use

Structured DFT is Preferred than Ad Hoc DFT


FFT

- Q: What do we do to control AND gate output to 1?

original

  


control x to 0

 

?


control x to 1

?

 


DFT - Part 1

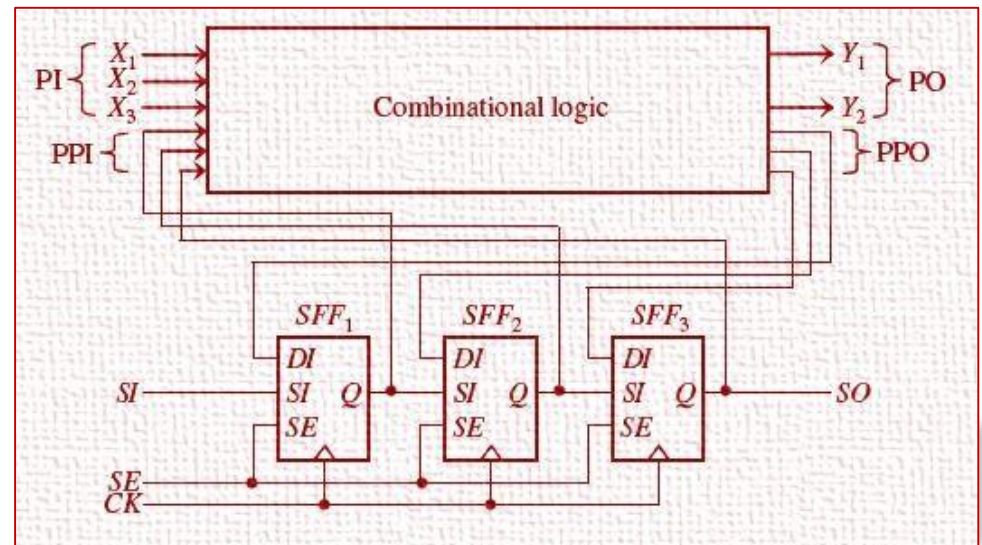- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - * Clocked scan (1968, NEC)
 - ◆ Latch-based
 - * LSSD (1977, IBM)
- Scan Design Flow
- Issues and Solutions
- Conclusion



Scan Chains

- Scan: connect (internal) FF/latches as shift register
 - ♦ Control and observe FF/latches **in test mode**
 - ♦ Remain original function **in normal mode**
- Proposed in early 1970's [Williams 73][Eichelberger 77]
 - ♦ **Most important DFT** for synchronous digital circuits
- **Scan chain insertion:** aka. **DFT insertion**, **DFT synthesis**
 - ♦ 1. Replace FF/latch 2. Stitch FF/latch into a chain

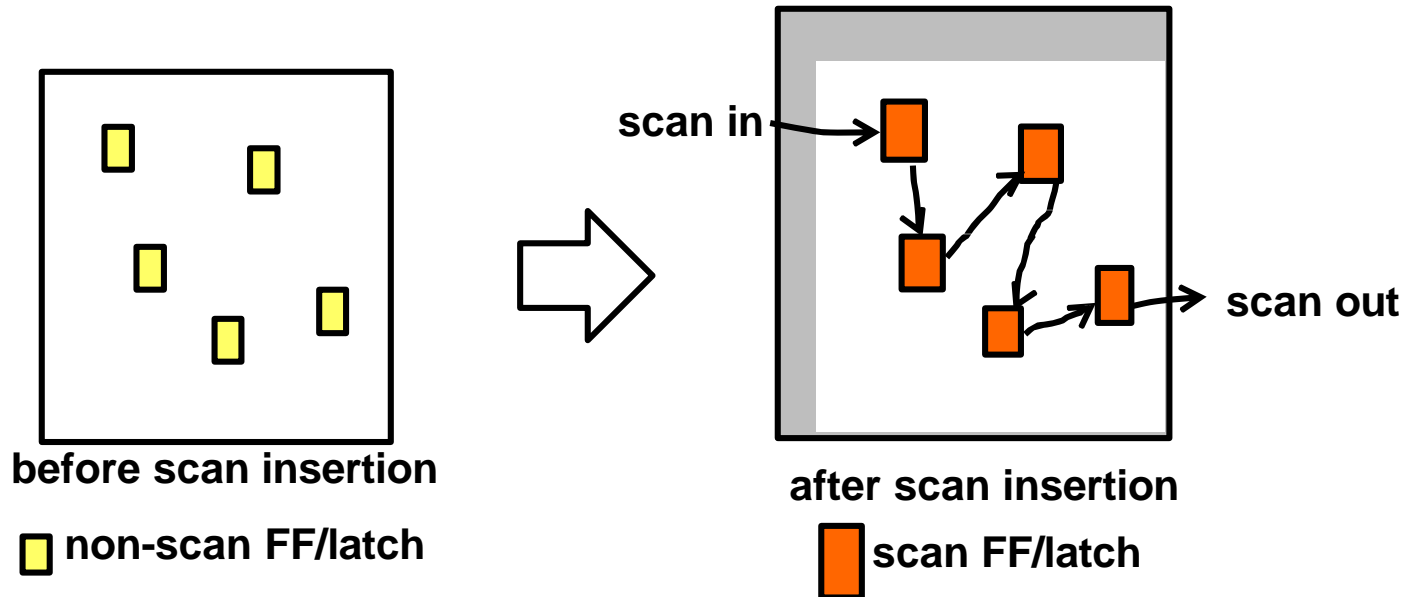


Scan Flip-Flop (SFF) *scan latch is similar


- SFF has four main pins:

- ♦ Scan Chain: **Scan Input (SI)**, **Scan output (SO)**
- ♦ Logic: **Data Input (DI)**, **Data Output (DO)**


* DO and SO can be shared

 

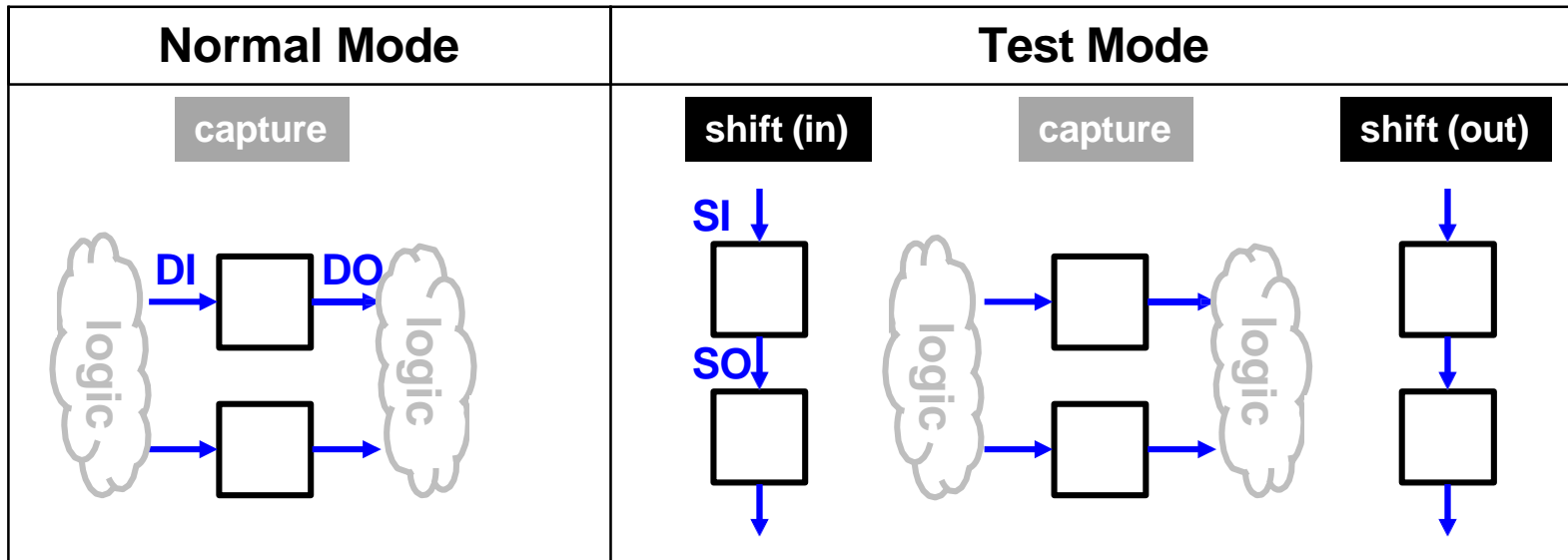- SFF has two functions: **shift** and **capture**
- Circuit has two operation modes: **Normal** mode and **Test** mode




Example: Scan Insertion

 

Example: Normal Mode

- Scan-FF same as non-scan FF

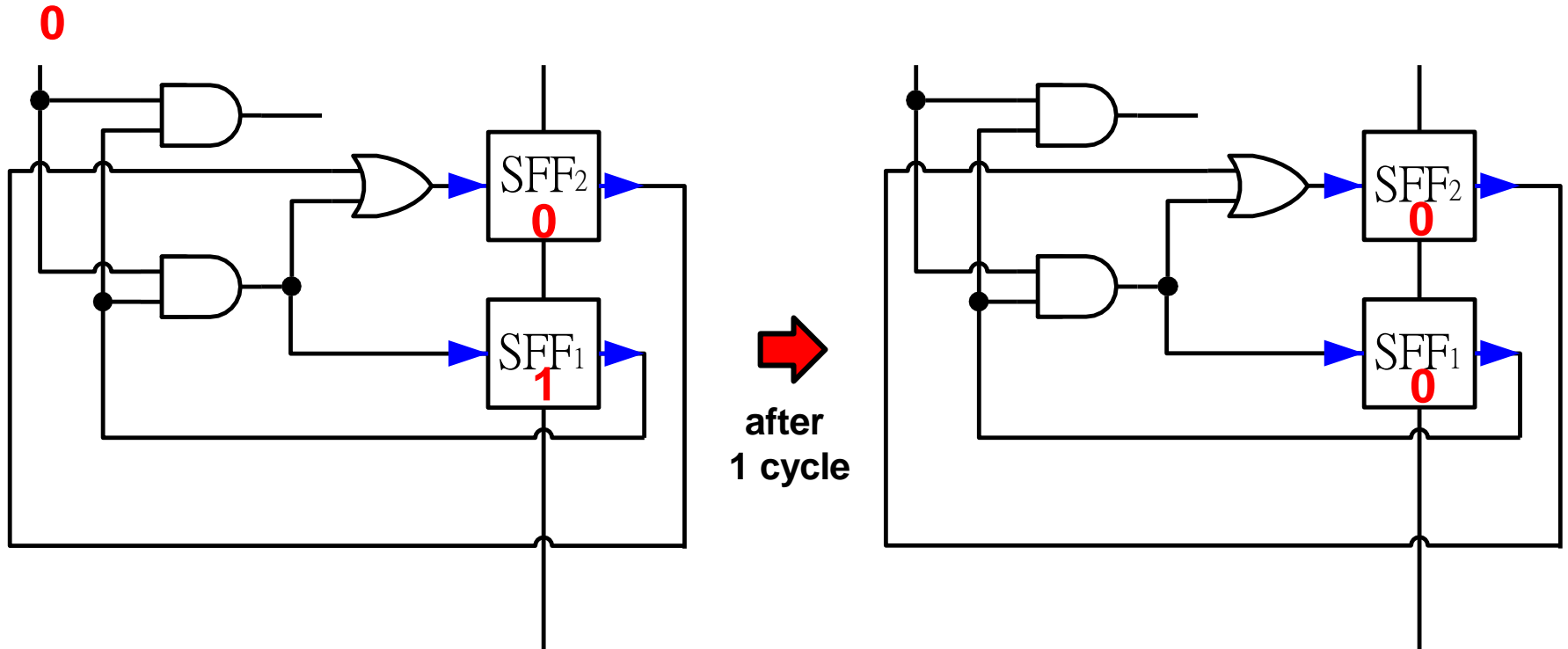

Example: Test Mode


Shift (in)
2 cycles




Capture
1 cycle




Shift (out)
2 cycles

 

 this figure shows
state of SFF after 2 cycles



 this figure shows
state of SFF after capture cycle



observed 1/0
at 2nd cycle


Fault Detected in Test Mode

NOTE: this fault untestable in Normal Mode. why?


Quiz

Q: Consider SA1 fault, please fill in values of ?


Shift (in)
after 2 cycles

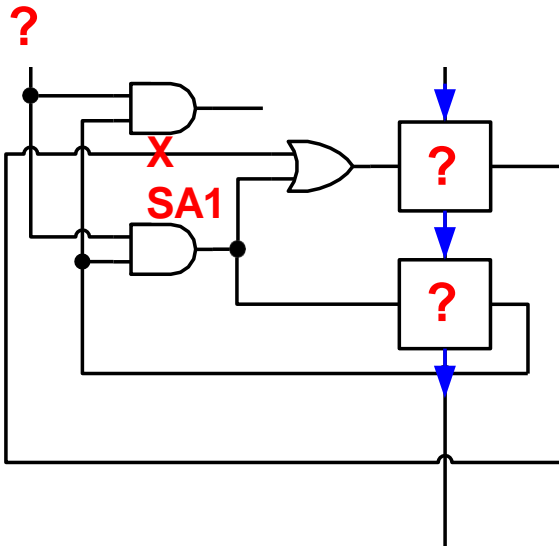

Capture
after 1 cycle

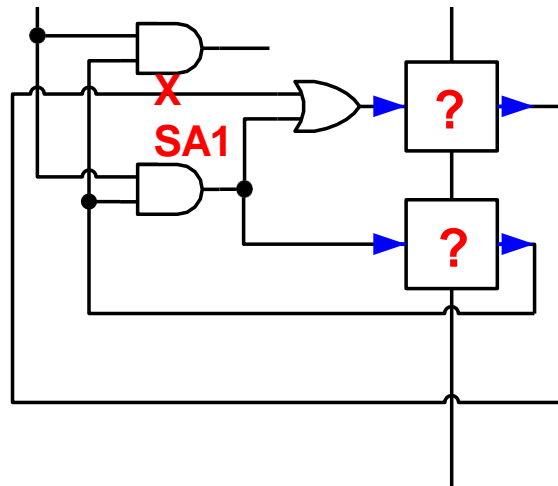



Shift (out)
after 2 cycles

 

observed ?
@ ? cycle

Scan Turns Seq. Ckt. to Comb. Ckt.

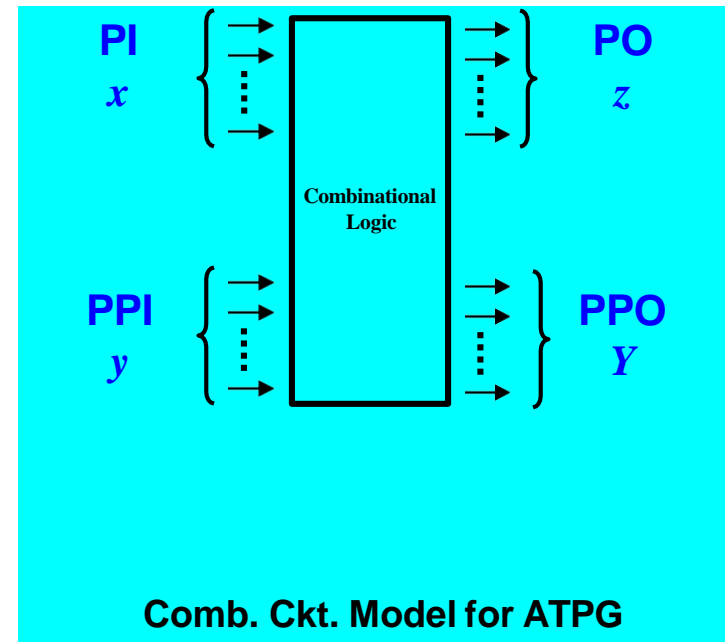 - Scan turns sequential ckt into combinational ckt in test mode
 - ♦ ATPG sees only **comb. ckt. model**
- SFF DO become **Pseudo Primary Input (PPI)**, fully controllable
- SFF DI become **Pseudo Primary Output (PPO)**, fully observable



Scan Makes ATPG Easier!



QUIZ

We insert scan into this circuit so we can remove FF in ATPG model.

Q1: Which pins are PI? PO? PPI? PPO?

Q2: If we want to detect SA0 fault, what are their values?

ANS:

 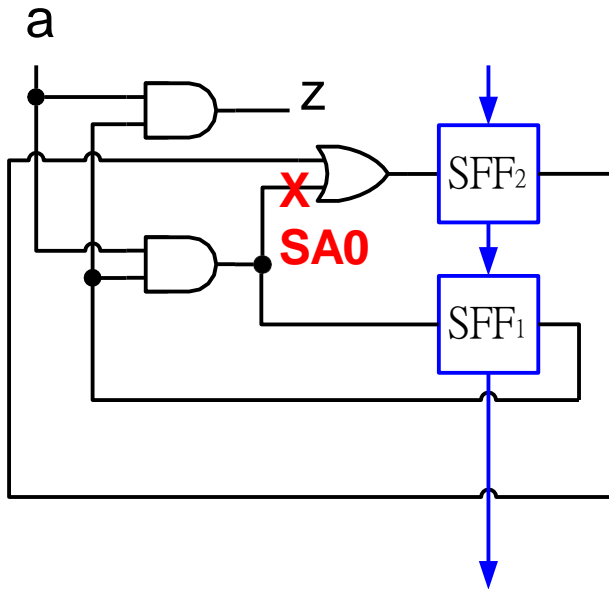


Pros and Cons of Scan

- Advantages of scan
 - ◆ **Systematic DFT**, not *ad hoc*. Many automatic tools.
 - ◆ **Easy ATPG**: faster run time and higher fault coverage
 - ◆ Easy **silicon debugging** or *diagnosis*
- Disadvantages of scan
 - ◆ **Area overhead** (typically, 5~10% OH acceptable)
 - * larger SFF area + routing for scan chains
 - ◆ **Performance overhead**
 - * SFF has longer setup time, hold time
 - ◆ **Pin overhead**
 - * scan in, scan out, *scan enable*, *scan clocks* ...
 - ◆ **Power overhead**
 - ◆ **Extra design efforts**
 - * scan insertion, verification

QUIZ

We insert scan into this circuit and replace non-scan FF by scan FF.

 Q: Given the gate area table, what is area overhead of scan DFT?




Gate	area
OR	3
AND	3
non-scan FF	5
scan FF	6

ANS:

$$\text{area O.H.} = \frac{\text{area}_{\text{afterDFT}} - \text{area}_{\text{beforeDFT}}}{\text{area}_{\text{beforeDFT}}} =$$


Summary

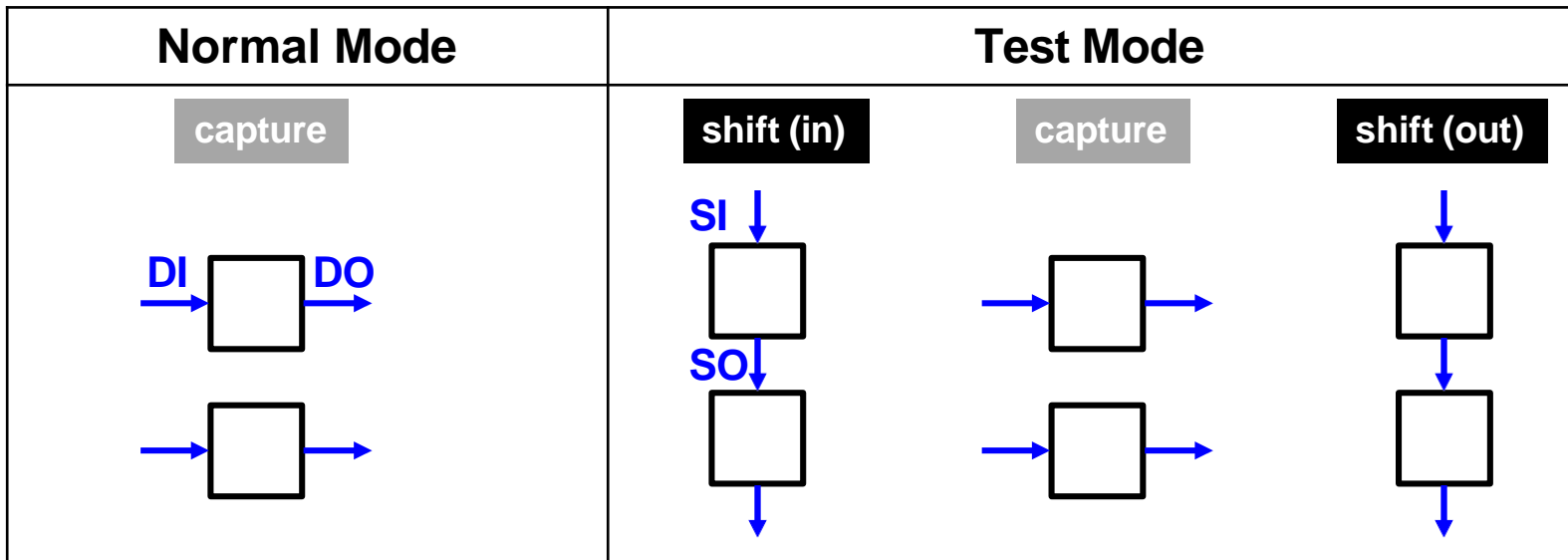- Scan is **most popular DFT** for digital VLSI
- Scan FF has four pins: **SI, SO, DI, DO**
- Circuit has two operation modes: **normal** mode, **test** mode
 - ♦ Test mode: **shift** (in), **capture**, **shift** (out)
- Scan makes ATPG easier at cost of **overhead** (area/performance ...)




FFT

 - Q1: This stuck-at zero fault is untestable in normal mode, why?
- Q2: Since it is untestable in normal mode, why do we care about it?




DFT - Part 1

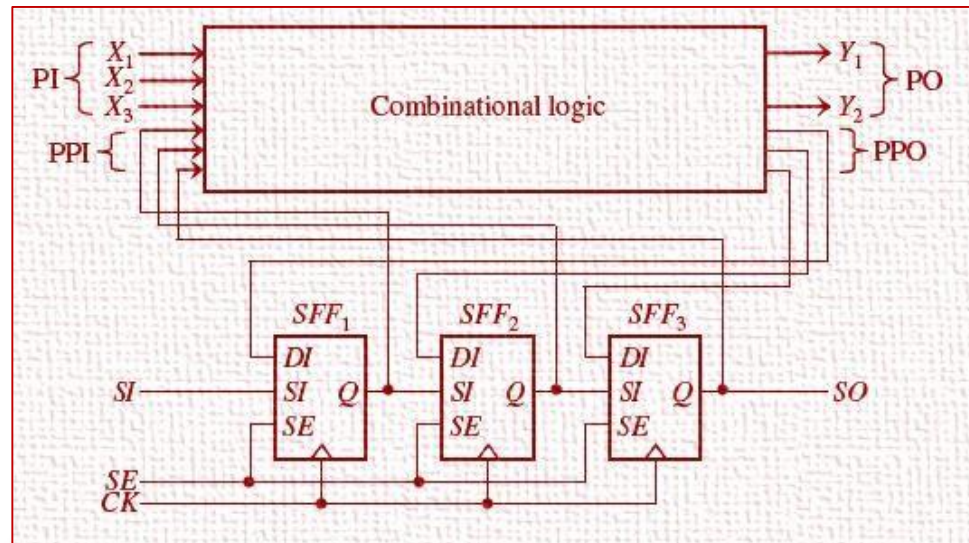- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - MUXed-D scan flip-flop
 - **Test Mode Operation**
 - * Clocked scan (1968, NEC)
 - * Other scan
 - ◆ Latch-based
 - * LSSD (1977, IBM)
- Scan Design Flow
- Issues and Solutions
- Conclusion




MUXed-D Scan Flip-flop [Williams 73]

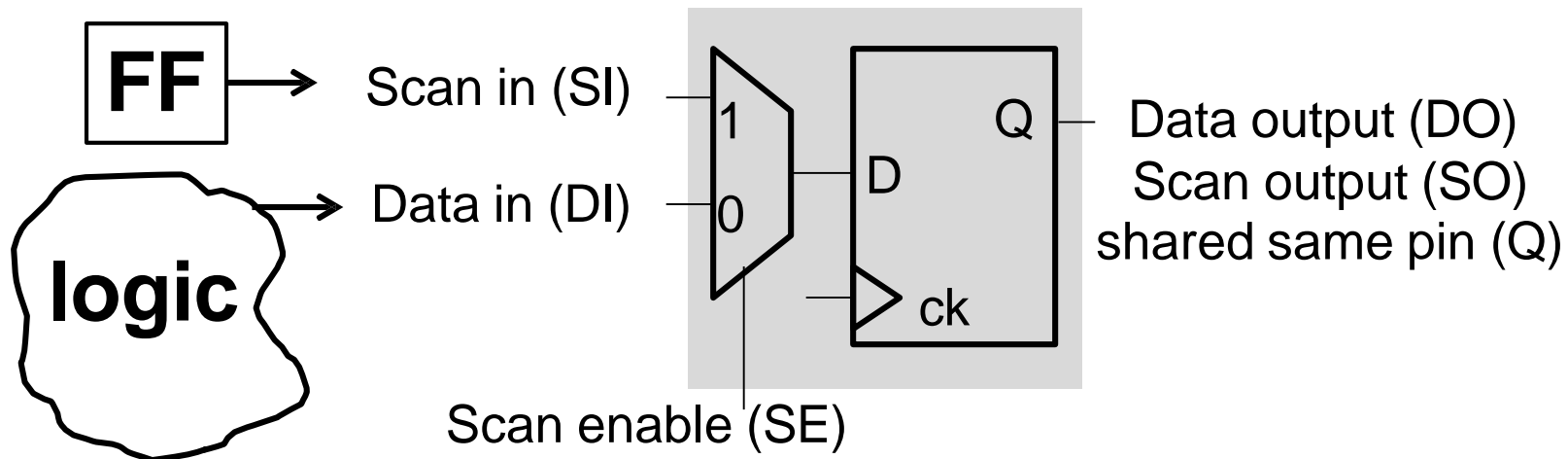- Often used in flip-flop based, standard cell design
- 3 input, 1 output, 1 clock pin
- **Scan Enable** (SE) pin selects inputs
 - ♦ **Data in** (DI): from logic
 - ♦ **Scan in** (SI): from previous scan FF
- **Data output** (DO) and **Scan output** (SO) often share same pin (Q)
- One multiplier (MUX) slower and larger than regular non-scan FF




MUXed-D Scan Flip-flop

 - Positive edge triggered MUXed-D scan FF
 - ♦ **SE=1**, $SI \rightarrow Q$ at positive clock edge
 - ♦ **SE=0**, $DI \rightarrow Q$ at positive clock edge





	operation
SE=0	Capture ($DI \rightarrow Q$)
SE=1	Shift ($SI \rightarrow SO$)

 


SE = 1 enables scan

Muxed-D Scan Architecture

 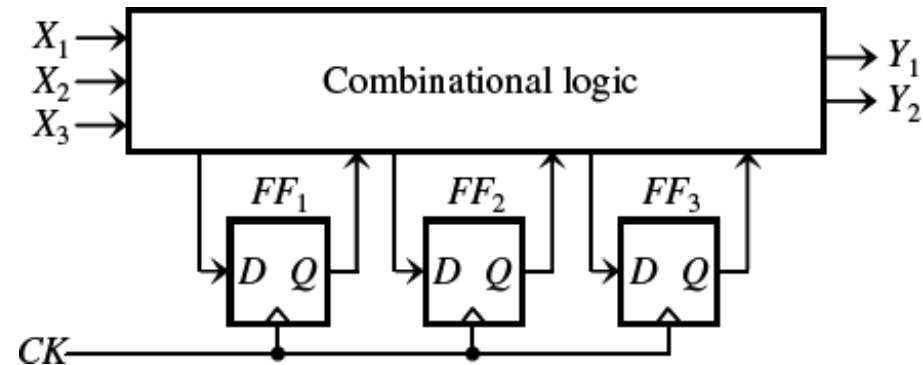- Original circuit
 - ♦ Single clock
 - ♦ Positive edge triggered
 - ♦ Non-scan DFF



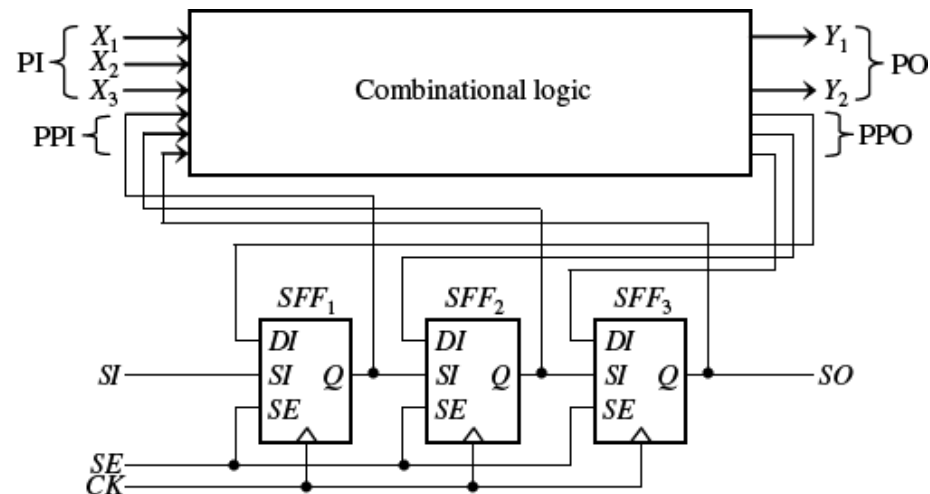- After scan insertion
 - ♦ Three extra pins
 - * **SI, SE, SO**




SFF = scan FF

Normal Mode Operation


- Always $SE = 0$
- Same as original circuit

	operation
SE=0	Capture ($DI \rightarrow Q$)
SE=1	Shift ($SI \rightarrow SO$)

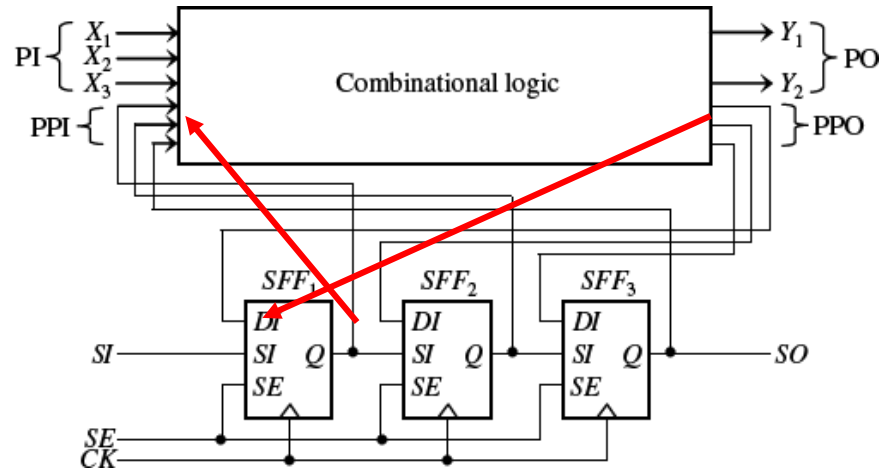


Test Mode Operation

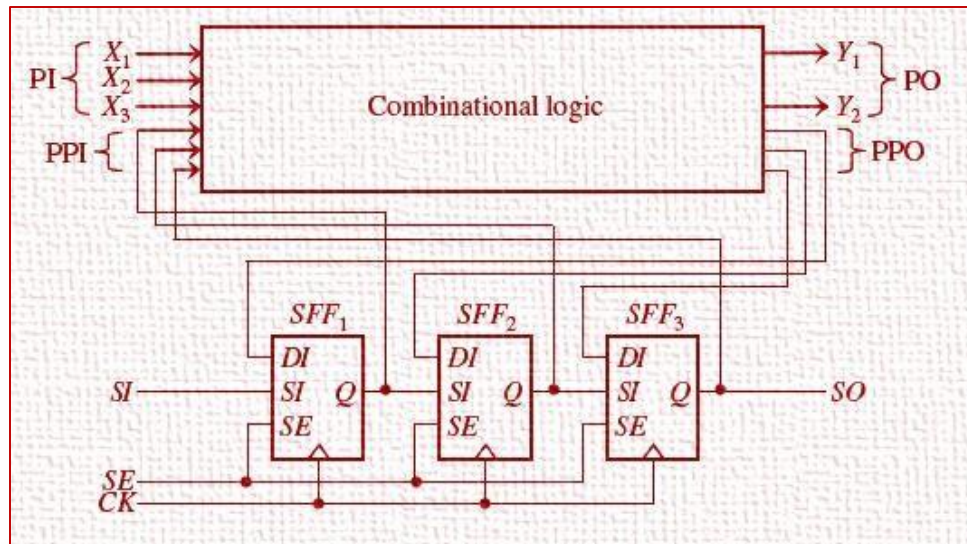- Stuck-at fault testing
 - ◆ One pattern per scan
- Delay fault testing
 - ◆ Two-patterns per scan
 - * Launch-on-Shift
 - * Lunch-on-Capture






DFT - Part 1

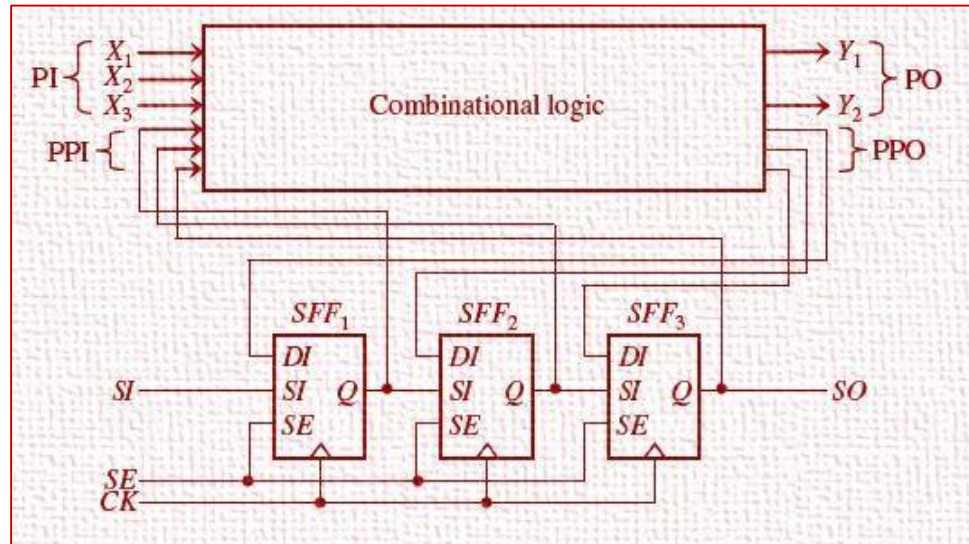- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - MUXed-D scan flip-flop
 - Test Mode Operation
 - Ckt. Model for ATPG
 - ◇ SSF
 - ◇ LOS
 - ◇ LOC
 - * Clocked scan
 - * Other scan
 - ◆ Latch-based





How to Run Comb. ATPG on Seq. Ckt?

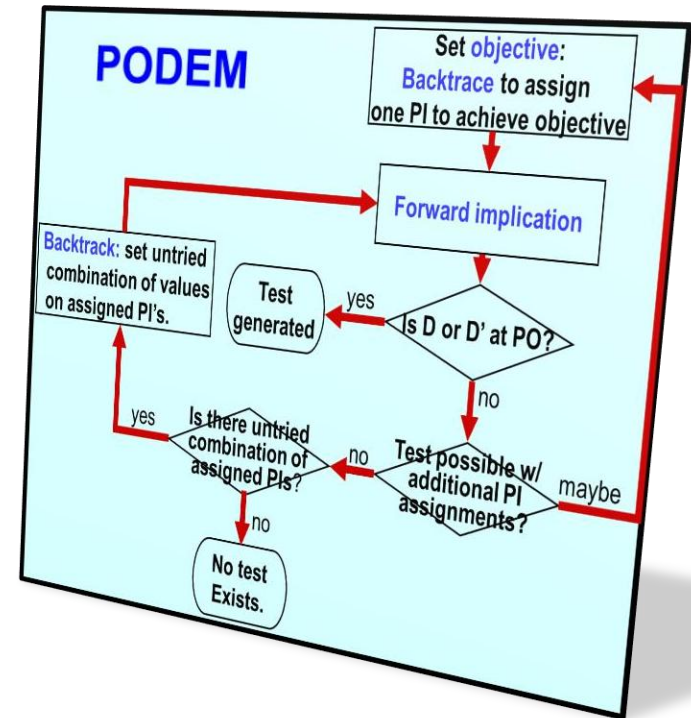  

DFT Turns Seq. Ckt. to Comb. Ckt.

 
 
- DFT turns sequential ckt into combinational ckt in test mode
 - ♦ ATPG sees only **comb. ckt. model**
- Scan FF become **Pseudo Primary Input (PPI)**, fully controllable
- Scan FF become **Pseudo Primary Output (PPO)**, fully observable



Comb. ATPG Much Faster than Seq. ATPG

  Example (1/2)

- Two scan FF in a scan chain
- $SI \rightarrow FF-B \rightarrow FF-C \rightarrow SO$




- A is **PI**
- B, C are **PPI**
- K is **PO**
- H, J are **PPO**
 - ♦ $H = B^{PPO}, J = C^{PPO}$

NOTE: this model assume no fault in FF. (see FFT)

 
Example (2/2)

- Generate SSF ATPG pattern
 - ◆ H SA0 fault



PI	PPI	PO	PPO
A	B ^{PPI} C ^{PPI}	K	B ^{PPO} C ^{PPO}
1	1 X	D'	D 0

comb. pattern

 


scan pattern

load	capture	unload
A=1	K=L	
SI=X1		SO=LH

Quiz

Q1: Convert seq. ckt. into comb. ckt. model for SSF ATPG.

 
Q2: Generate a test pattern for SA1 fault.
(show comb. pattern)



PI	PPI	PO	PPO
a	y ₁ y ₂	z	Y ₁ Y ₂



DFT - Part 1

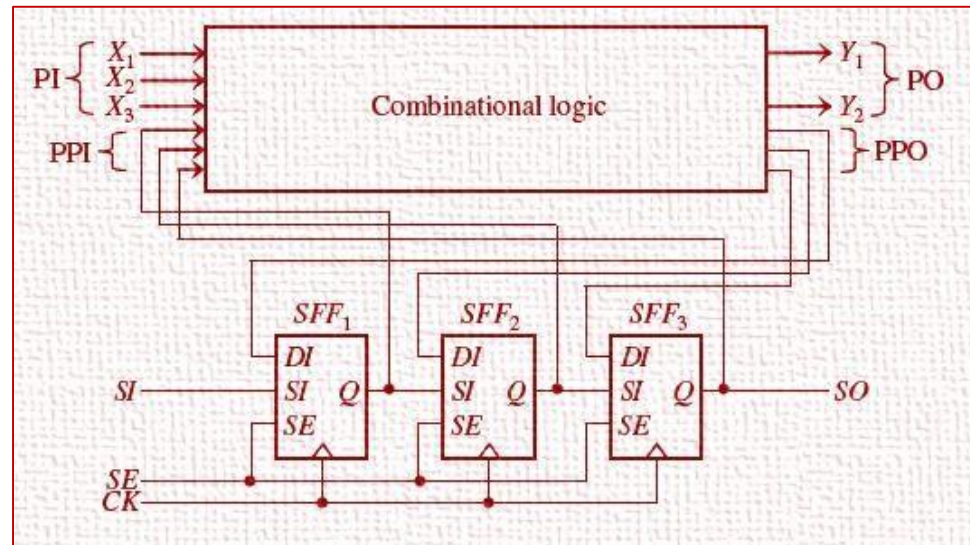- Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - * Clocked scan (1968, 1975 NEC)
 - * Other scan
 - ◆ Latch-based
 - * LSSD (1977, IBM)
- Scan Design Flow
- Issues and Solutions
- Conclusion



Clocked Scan FF [Kobayashi 68][Funatsu 75]

  
- 2 inputs
 - ♦ Data in (**DI**): from logic
 - ♦ Scan in (**SI**): from previous scan FF
- 2 independent clocks
 - ♦ Scan clock (**SCK**): capture **SI**
 - ♦ Data clock (**DCK**): capture **DI**
- Data output (**Q**) and Scan Output (**SO**) share same pin



IEEE symbol

Clocked Scan FF (2)

 - $DI \rightarrow Q$ at positive DCK edge
- $SI \rightarrow Q$ at positive SCK edge





(WWW. Fig 2.11)

SCK/DCK Do NOT Overlap


Clocked Scan Architecture

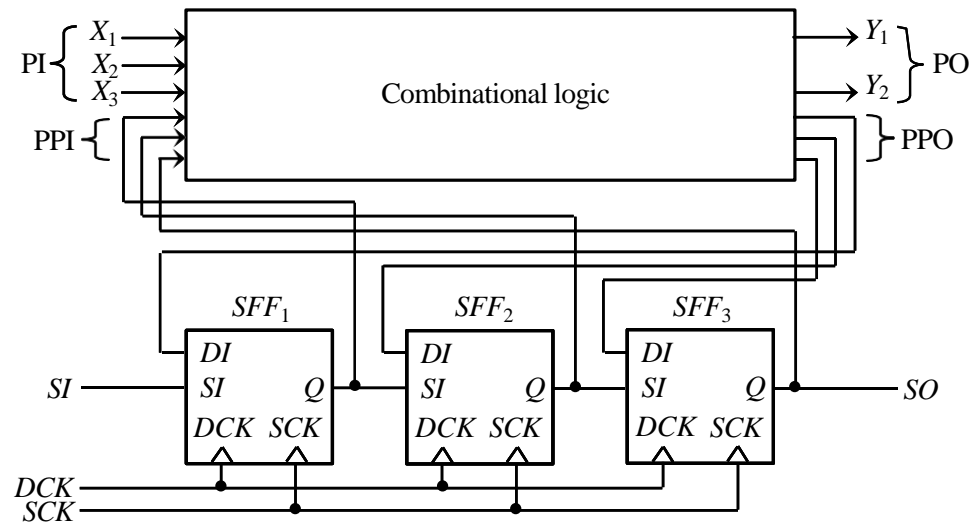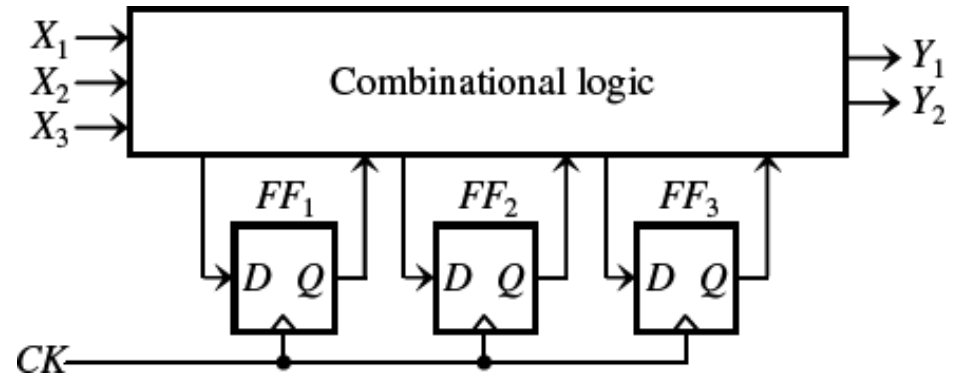- Original circuit
 - ♦ Single clock: CK
 - ♦ Regular D-FF
- After scan insertion
 - ♦ Two extra I/O pins
 - * SI, scan input
 - * SO, scan output
 - ♦ One extra clock
 - * SCK



Clocked Scan Operation

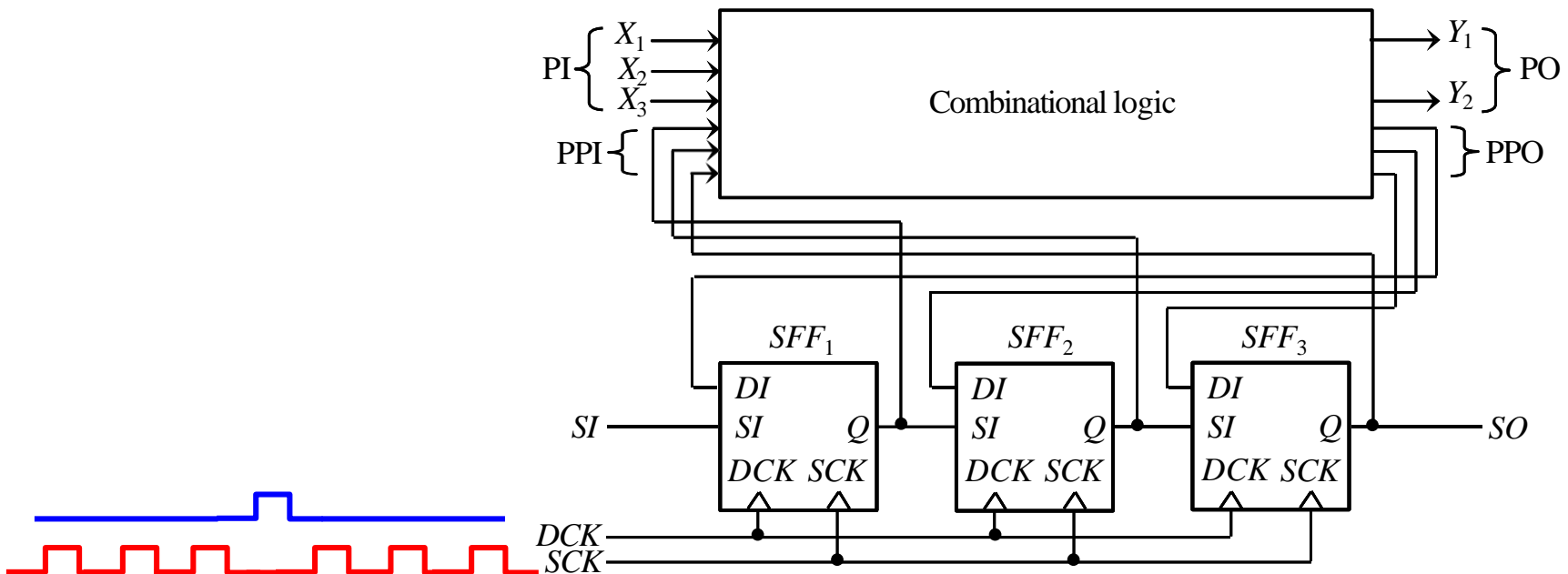- Normal Mode
 - ♦ DCK, DCK ...
- Test Mode
 - ♦ Shift: **SCK, SCK, SCK** (load scan chain)
 - ♦ Capture: **DCK**
 - ♦ Shift: **SCK, SCK, SCK** (unload scan chain)




Pros/Cons of Clocked Scan

- **Advantage**


- ♦ **Faster** than MUXed-D scan
 - * **Less delay overhead**

- **Disadvantage**

 - ♦ **Larger routing overhead** than MUXed-D scan
 - * **Needs one extra clock distribution (SCK)**



MUXed-D scan

 

Clocked scan

CS Faster but Larger

Quiz


Q: Which of the following is NOT true about clocked scan?

- A. Clocked scan is better than MUXed-D scan**
- B. Clocked scan has two clocks**
- C. Clocked scan is faster than MUXed-D scan**
- D. Clocked scan is useful for high speed circuits**


ANS:

APPENDIX: Schematic of MUXed-D Scan

(BA Fig. 14.2)

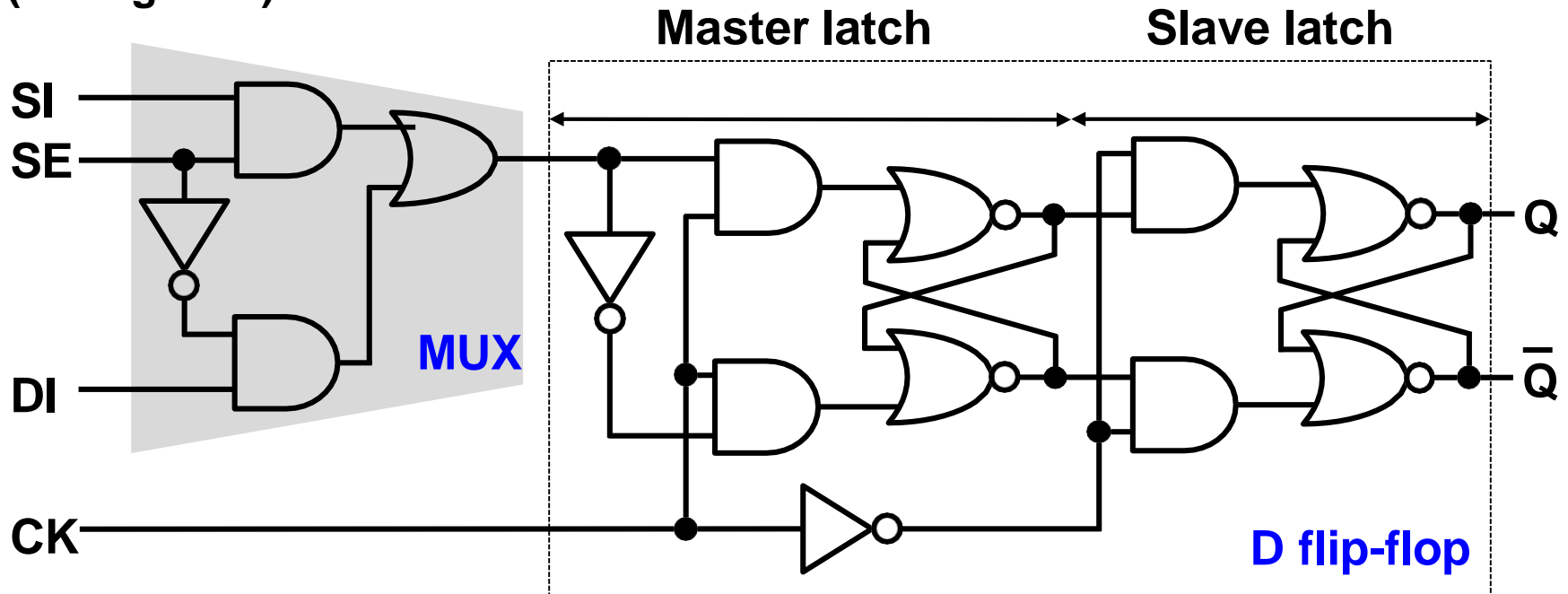


APPENDIX: Schematic of Clocked Scan

 

DFT - Part 1

 - Introduction
- Internal Scan
 - ◆ FF-based
 - * MUXed-D scan (1973, Stanford)
 - * Clocked scan (1968, NEC)
 - * Other scan
 - ◆ Latch-based
 - * LSSD (1977, IBM)
- Scan Design Flow
- Issues and Solutions
- Conclusion



Reference

- [Eichelberger 77] E.B. Eichelberger, and T.W. Williams, "A logic design structure for LSI testability." Proc. of Design Auto. Conf., 1977. (IBM)
- [Funatsu 75] S. Funatsu, N. Wakatsuki, and T. Arima, "Test generation systems in Japan," Proc. Design Auto. Symp., 1975. (NEC)
- [Kobayashi 68] A. Kobayashi, S Matsue, H Shiba "Flip-flop circuit with FLT capability," Proc. of IECEO conf., 1968. (NEC)
- [McCluskey 86] E. J. McCluskey , *Logic Design Principles*, 1986
- [Williams 73] M.J.Y. Williams, J. B. Angell, "Enhancing Testability of Large-Scale Integrated Circuits via Test Points and Additional Logic," IEEE Trans. on Comput., Vol. C-22, Issue: 1, 1973. (Stanford)